

# **CSC 252: Computer Organization**

## **Spring 2022: Lecture 11**

Instructor: Yuhao Zhu

Department of Computer Science  
University of Rochester

# Announcements


- Programming assignment 3 is out
  - Details: <https://www.cs.rochester.edu/courses/252/spring2022/labs/assignment3.html>
  - Due on **March 3**, 11:59 PM
  - You (may still) have 3 slip days

13	14	15	16	17 Today	18	19
20	21	22	23	24	25	26
27	28	Mar 1	2	3 Due Mid-term	4	5

# Announcements

- Grades for Lab 1 are posted.
- We are processing regrading requests
- Will grade Lab 2 soon.
  
- Programming assignment 3 is in x86 assembly language. Seek help from TAs.
- TAs are best positioned to answer your questions about programming assignments!!!
- Programming assignments do NOT repeat the lecture materials. They ask you to synthesize what you have learned from the lectures and work out something new.

# So far in 252...

 


# Today: Circuits Basics

- Basics
- Circuits for computations
- Circuits for storing data
 
# Overview of Circuit-Level Design


- Fundamental Hardware Requirements
  - Communication: How to get values from one place to another. Mainly three electrical **wires**.
  - Computation: **transistors**. Combinational logic.
  - Storage: **transistors**. Sequential logic.
- Circuit design is often abstracted as **logic design**



# Today: Circuits Basics


- Transistors
- Circuits for computations
- Circuits for storing data

# Inverter (NOT Gate)

 






# Inverter (NOT Gate)

 




# Inverter (NOT Gate)

 


# Inverter (NOT Gate)

  



# Inverter (NOT Gate)

   



# Inverter (NOT Gate)

 

In	Out
0	1
1	0

  


# NOR Gate (NOT + OR)

  


A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

Note: Serial structure on top, parallel on bottom.


# Basic Logic Gates

 


*NOT*

 


*OR*

 

*NOR*

 


*AND*

 

*NAND*


# Computing with Logic Gates

And

 


$$\text{out} = a \ \&\& \ b$$

Or

 


$$\text{out} = a \ || \ b$$

Not

 


$$\text{out} = !a$$

 - Outputs are Boolean functions of inputs
- Respond continuously to changes in inputs **with some small delay**
- **Different gates have different delays (b/c different transistor combinations)**







# Computing with Logic Gates

 

 
- Outputs are Boolean functions of inputs
- Respond continuously to changes in inputs **with some small delay**
- **Different gates have different delays (b/c different transistor combinations)**




# Computing with Logic Gates

 

 
- Outputs are Boolean functions of inputs
- Respond continuously to changes in inputs **with some small delay**
- **Different gates have different delays (b/c different transistor combinations)**




# Computing with Logic Gates

 

 - Outputs are Boolean functions of inputs
- Respond continuously to changes in inputs **with some small delay**
- **Different gates have different delays (b/c different transistor combinations)**




# Combinational Circuits

 


- A Network of Logic Gates
  - Continuously responds to changes on primary inputs
  - Primary outputs become (**after some delay**) Boolean functions of primary inputs

# Bit Equality


# Bit Equality

 

# Bit Equality

 


# Bit Equality

 





# Bit Equality

 


# Bit Equality

 


# Bit Equality

 


# Bit Equality

 

# Bit Equality

 


# Delay of Bit Equal Circuit

 


- What's the delay of this bit equal circuit?
  - Assuming 1-input NOT takes 1 unit of time, 2-input AND takes 4.3, and 2-input OR takes 4.7

# Delay of Bit Equal Circuit

 

- What's the delay of this bit equal circuit?
  - Assuming 1-input NOT takes 1 unit of time, 2-input AND takes 4.3, and 2-input OR takes 4.7


# Delay of Bit Equal Circuit

 

- What's the delay of this bit equal circuit?
  - Assuming 1-input NOT takes 1 unit of time, 2-input AND takes 4.3, and 2-input OR takes 4.7
- The delay of a circuit is determined by its “critical path”
  - The path between an input and the output that the maximum delay
  - Estimating the critical path delay is called static timing analysis





# Delay of Bit Equal Circuit


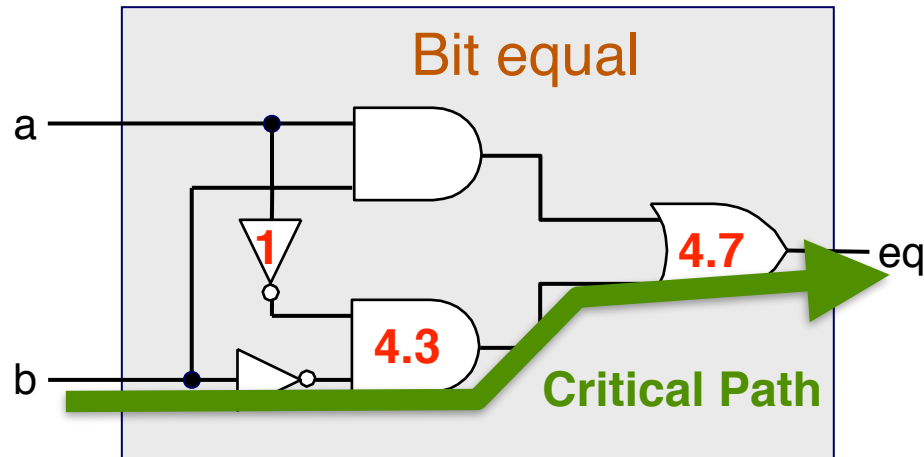


- What's the delay of this bit equal circuit?
  - Assuming 1-input NOT takes 1 unit of time, 2-input AND takes 4.3, and 2-input OR takes 4.7
- The delay of a circuit is determined by its “critical path”
  - The path between an input and the output that the maximum delay
  - Estimating the critical path delay is called static timing analysis


# Glitch/Hazard

  


# Glitch/Hazard

  


# Glitch/Hazard

 

 
- A glitch is an unnecessary signal transition without functionality.





# Glitch/Hazard

 

 - A glitch is an unnecessary signal transition without functionality.
- Why is it bad? When transistors switch they consume power, but the power consumed during a glitch is a waste.




# Glitch/Hazard

 
 


- A glitch is an unnecessary signal transition without functionality.
- Why is it bad? When transistors switch they consume power, but the power consumed during a glitch is a waste.
- Without care, glitch power dissipation is 20%-70% of total power dissipation.

# 64-bit Equality

 


# 64-bit Equality

  



 
# Bit-Level Multiplexor (MUX)

- Control signal  $s$
- Data signals  $A$  and  $B$
- Output  $A$  when  $s=1$ ,  $B$  when  $s=0$


 
# Bit-Level Multiplexor (MUX)


- Control signal  $s$
- Data signals  $A$  and  $B$
- Output  $A$  when  $s=1$ ,  $B$  when  $s=0$




```
bool out = (s&&a) || (!s&&b)
```
 
# Bit-Level Multiplexor (MUX)

- Control signal  $s$
- Data signals  $A$  and  $B$
- Output  $A$  when  $s=1$ ,  $B$  when  $s=0$



```
bool out = (s&&a) || (!s&&b)
```

 


# 4-Input Multiplexor

- Control signal  $s$ ; Data signals A, B, C, and D
- Output: A when  $s = 00$ , B when  $s = 01$ , C when  $s = 10$ , D when  $s = 11$

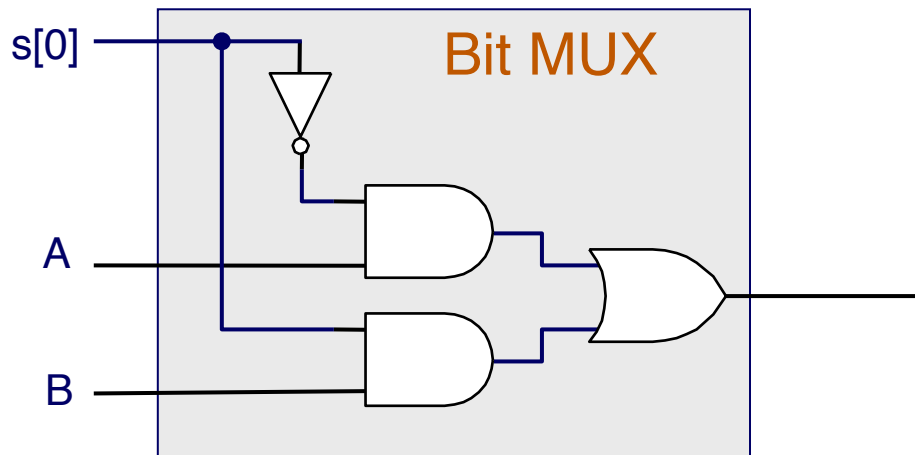
# 4-Input Multiplexor

- Control signal  $s$ ; Data signals A, B, C, and D
- Output: A when  $s = 00$ , B when  $s = 01$ , C when  $s = 10$ , D when  $s = 11$



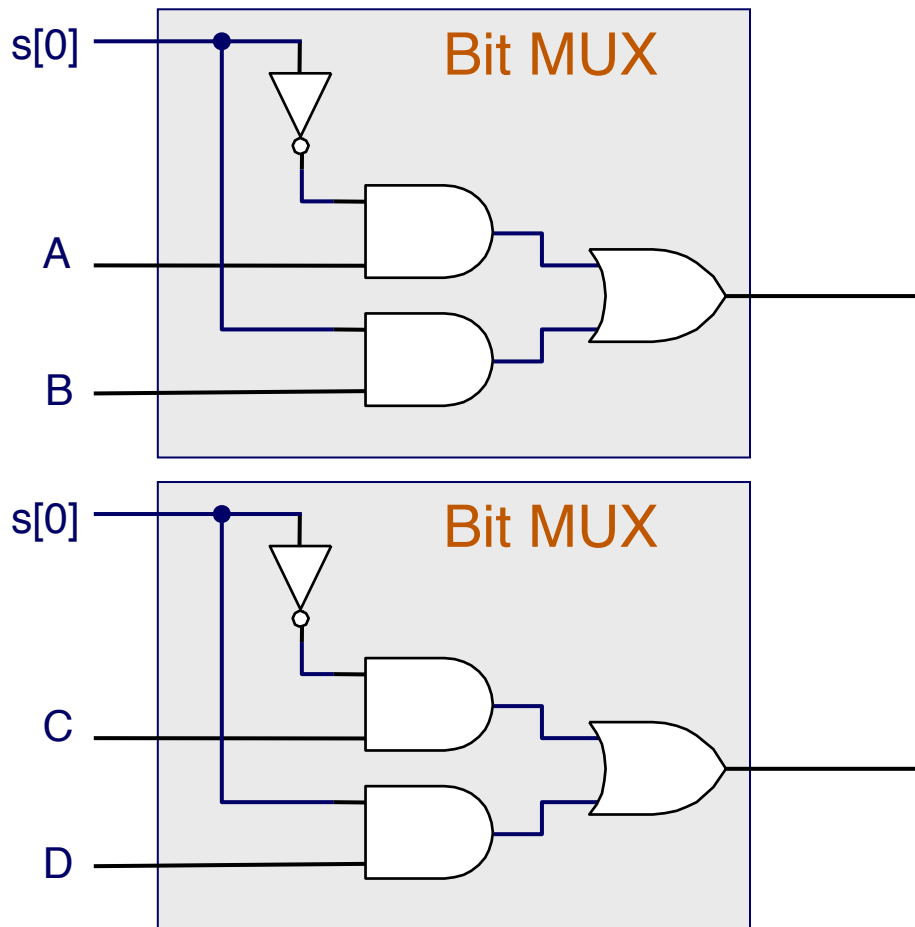
# 4-Input Multiplexor

- Control signal  $s$ ; Data signals A, B, C, and D
- Output: A when  $s = 00$ , B when  $s = 01$ , C when  $s = 10$ , D when  $s = 11$



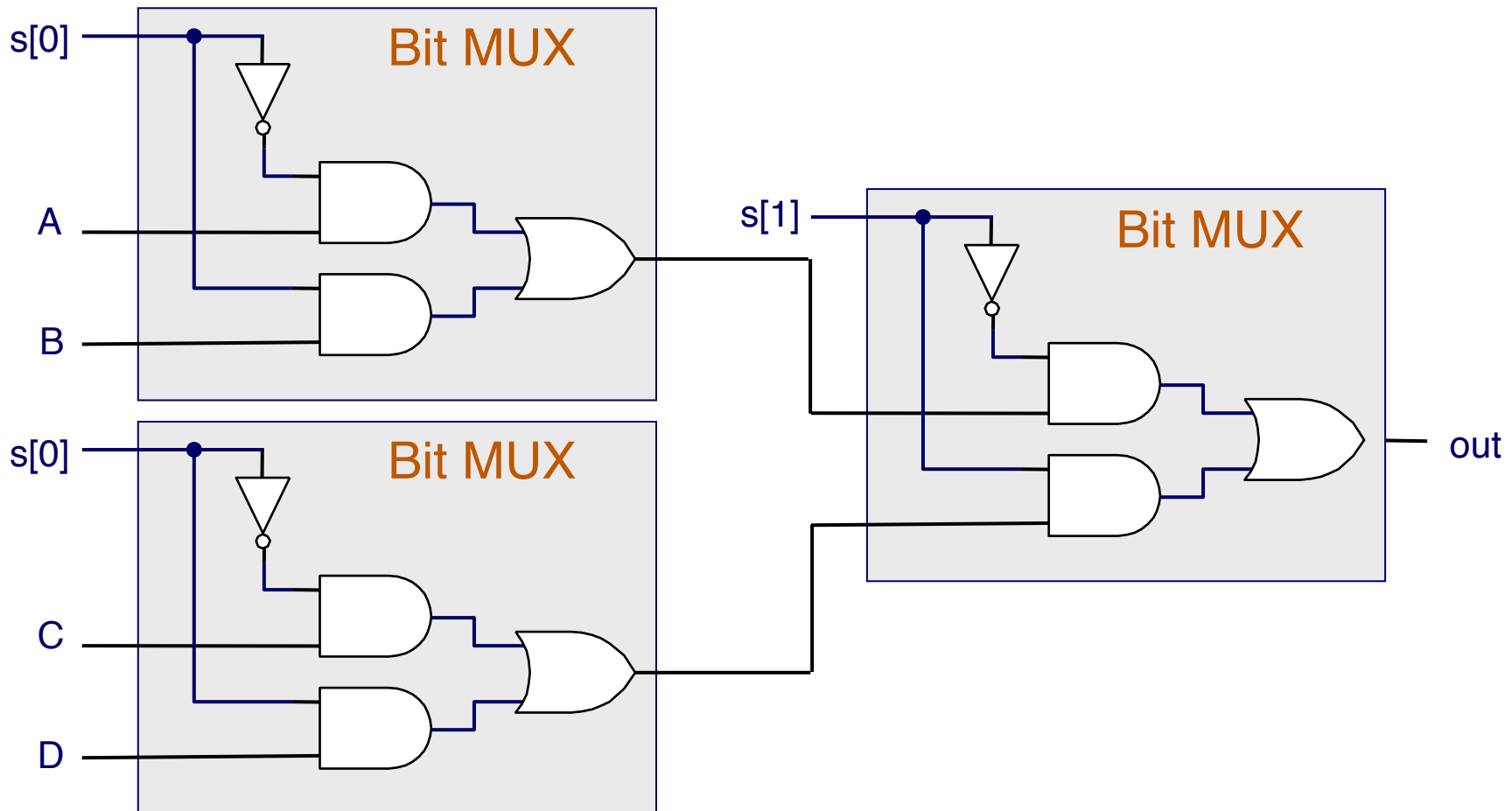
# 4-Input Multiplexor

- Control signal  $s$ ; Data signals A, B, C, and D
- Output: A when  $s = 00$ , B when  $s = 01$ , C when  $s = 10$ , D when  $s = 11$


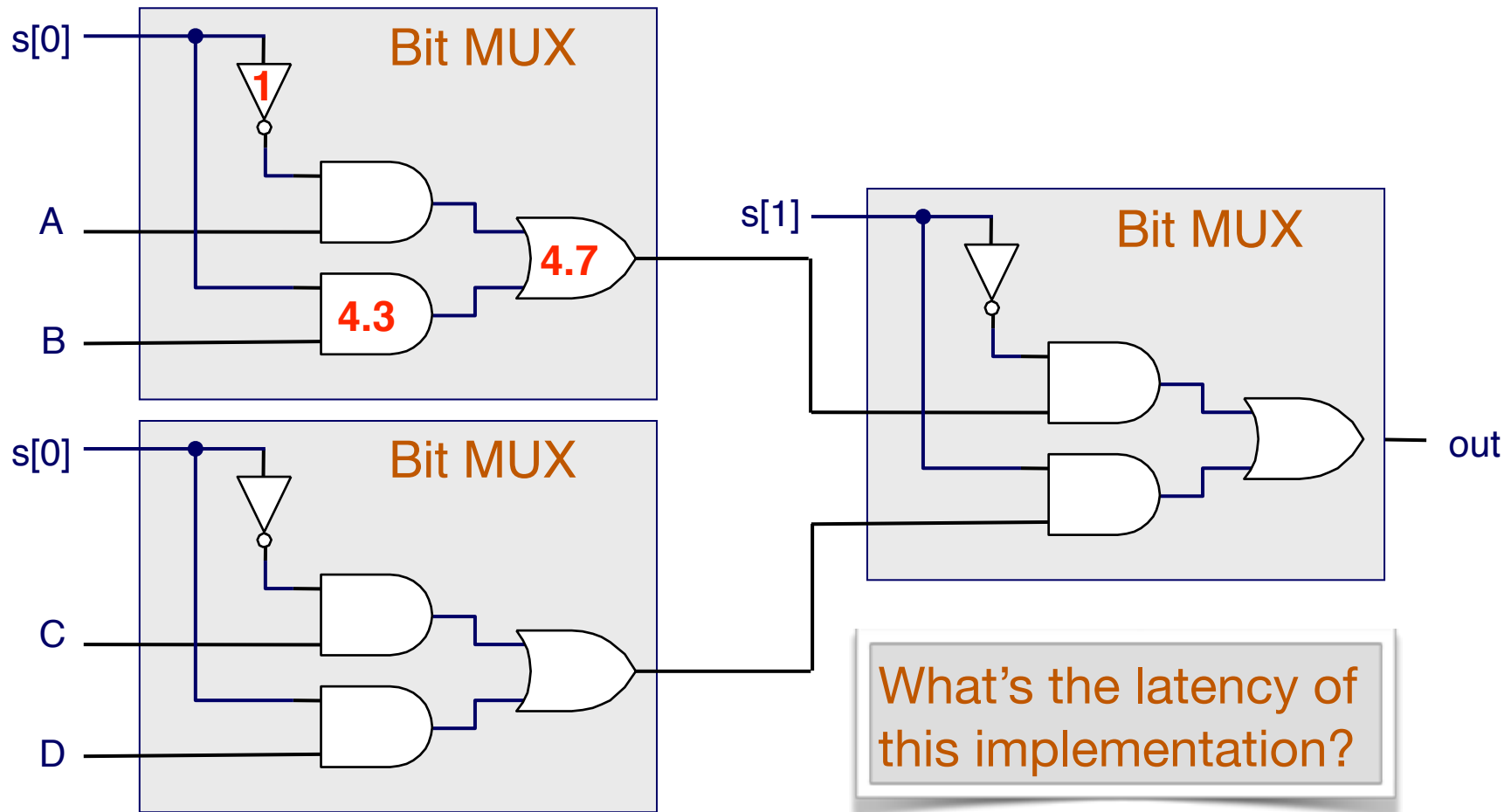
# 4-Input Multiplexor

- Control signal  $s$ ; Data signals A, B, C, and D
- Output: A when  $s = 00$ , B when  $s = 01$ , C when  $s = 10$ , D when  $s = 11$





# Logic Design and VLSI

- The number of inputs of a gate (fan-in) and the number of outputs of a gate (fan-out) will affect the gate delay.

# Logic Design and VLSI

- The number of inputs of a gate (fan-in) and the number of outputs of a gate (fan-out) will affect the gate delay.
- Think of logic gates as LEGOs, using which you generate the gate level circuit design for complex functionalities.

# Logic Design and VLSI

- The number of inputs of a gate (fan-in) and the number of outputs of a gate (fan-out) will affect the gate delay.
- Think of logic gates as LEGOs, using which you generate the gate level circuit design for complex functionalities.
- A standard cell library is a collection of well defined and appropriately characterized logic gates (delay, operating voltage, etc.) that can be used to implement a digital design.

# Logic Design and VLSI

- The number of inputs of a gate (fan-in) and the number of outputs of a gate (fan-out) will affect the gate delay.
- Think of logic gates as LEGOs, using which you generate the gate level circuit design for complex functionalities.
- A standard cell library is a collection of well defined and appropriately characterized logic gates (delay, operating voltage, etc.) that can be used to implement a digital design.
- The *logic synthesis tool* will automatically generate the “best” gate-level implementation of a piece of logic.

# Logic Design and VLSI

- The number of inputs of a gate (fan-in) and the number of outputs of a gate (fan-out) will affect the gate delay.
- Think of logic gates as LEGOs, using which you generate the gate level circuit design for complex functionalities.
- A standard cell library is a collection of well defined and appropriately characterized logic gates (delay, operating voltage, etc.) that can be used to implement a digital design.
- The *logic synthesis tool* will automatically generate the “best” gate-level implementation of a piece of logic.
- Take a Logic Design or Very Large Scale Integrated-Circuit (VLSI) course if you want to know more about circuit design.
  - Logic design uses the gate-level abstractions
  - VLSI tells you how the gates are implemented at transistor-level

# Recall: Full (1-bit) Adder

Add two bits and carry-in,  
produce one-bit sum and carry-out.

<b>A</b>	<b>B</b>	<b>C<sub>in</sub></b>	<b>S</b>	<b>C<sub>ou</sub></b>
				<b>t</b>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

# Recall: Full (1-bit) Adder

Add two bits and carry-in,  
produce one-bit sum and carry-out.

$$\begin{aligned} S = & (\sim A \ \& \ \sim B \ \& \ C_{in}) \\ & | (\sim A \ \& \ B \ \& \ \sim C_{in}) \\ & | (A \ \& \ \sim B \ \& \ \sim C_{in}) \\ & | (A \ \& \ B \ \& \ C_{in}) \end{aligned}$$

$$\begin{aligned} C_{ou} = & (\sim A \ \& \ B \ \& \ C_{in}) \\ & | (A \ \& \ \sim B \ \& \ C_{in}) \\ & | (A \ \& \ B \ \& \ \sim C_{in}) \\ & | (A \ \& \ B \ \& \ C_{in}) \end{aligned}$$

A	B	C <sub>in</sub>	S	C <sub>ou</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

# Recall: 1-bit Full Adder

Add two bits and carry-in,  
produce one-bit sum and carry-out.

$$\begin{aligned} C_{ou} = & (\sim A \& B \& C_{in}) \\ & | (A \& \sim B \& C_{in}) \\ & | (A \& B \& \sim C_{in}) \\ & | (A \& B \& C_{in}) \end{aligned}$$



# Recall: 1-bit Full Adder


$$C_{ou} = (\sim A \& B \& C_{in})$$

$$| (A \& \sim B \& C_{in})$$

$$| (A \& B \& \sim C_{in})$$

$$| (A \& B \& C_{in})$$

 
Add two bits and carry-in,  
produce one-bit sum and carry-out.



 
# Recall: 1-bit Full Adder

$$C_{ou} = (\sim A \& B \& C_{in}) \mid (A \& \sim B \& C_{in}) \mid (A \& B \& \sim C_{in}) \mid (A \& B \& C_{in})$$

Add two bits and carry-in,  
produce one-bit sum and carry-out.




# Recall: Four-bit Adder

 

 
# Recall: Four-bit Adder

- Ripple-carry Adder
  - Simple, but performance linear to bit width



 
# Recall: Four-bit Adder

- Ripple-carry Adder
  - Simple, but performance linear to bit width
- Carry look-ahead adder (CLA)
  - Generate all carriers simultaneously




# Arithmetic Logic Unit

 

- An ALU performs multiple kinds of computations.
- The actual computation depends on the selection signal  $s$ .
- Also sets the condition codes (status flags)
- For instance:
  - $X + Y$  when  $s == 00$
  - $X - Y$  when  $s == 01$
  - $X \& Y$  when  $s == 10$
  - $X \wedge Y$  when  $s == 11$
- How can this ALU be implemented?
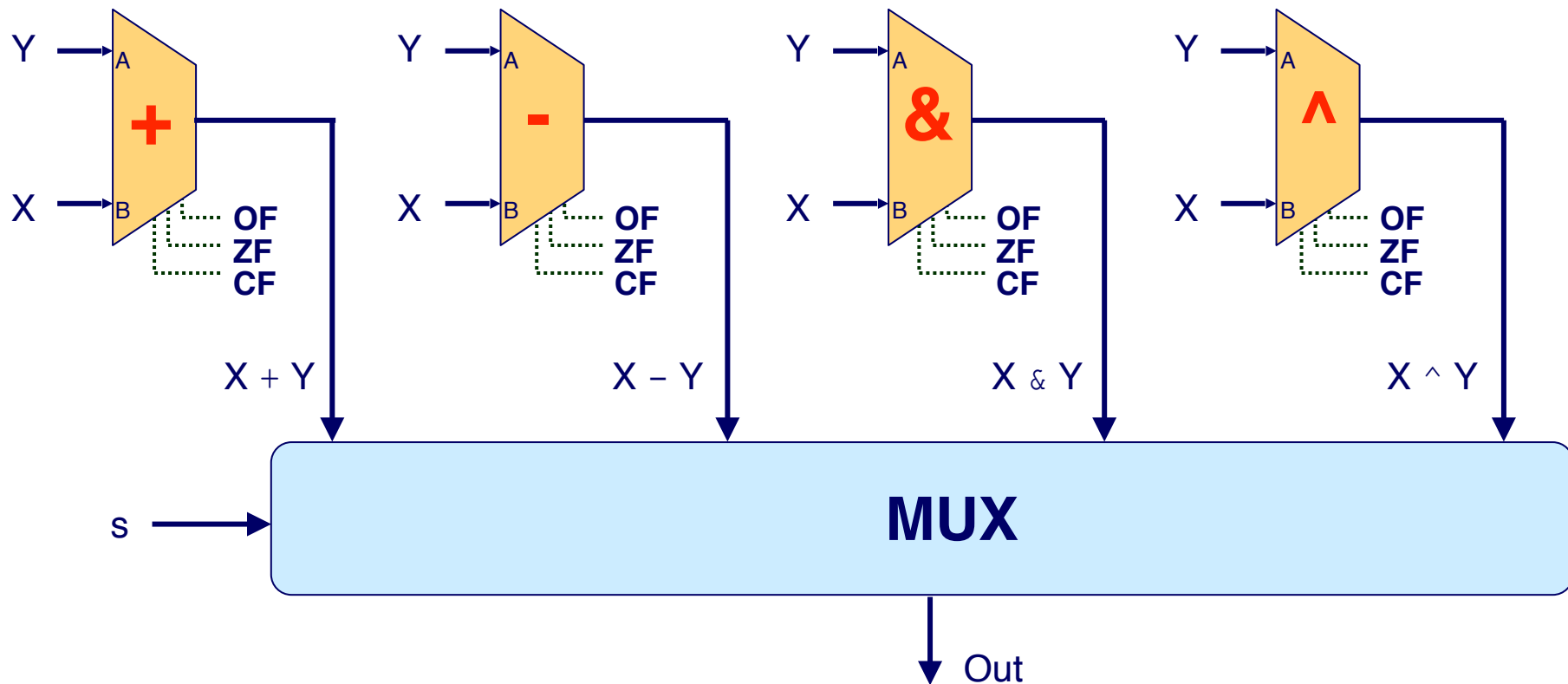
# Arithmetic Logic Unit

- Implement 4 different circuits, one for each operation.
- Then use a MUX to select the results



# Today: Circuits Basics

- Transistors
- Circuits for computations
- Circuits for storing data



# The Need for Storing Bits

- Assembly programs set architecture (processor) states.
  - Register File
  - Status Flags
  - Memory
  - Program Counter

# The Need for Storing Bits

- Assembly programs set architecture (processor) states.
  - Register File
  - Status Flags
  - Memory
  - Program Counter
- Every state is essentially some bits that are stored/loaded.

# The Need for Storing Bits

- Assembly programs set architecture (processor) states.
  - Register File
  - Status Flags
  - Memory
  - Program Counter
- Every state is essentially some bits that are stored/loaded.
- Think of the program execution as an FSM.


# The Need for Storing Bits

- Assembly programs set architecture (processor) states.
  - Register File
  - Status Flags
  - Memory
  - Program Counter
- Every state is essentially some bits that are stored/loaded.
- Think of the program execution as an FSM.
- The hardware must provide mechanisms to load and store bits.

# The Need for Storing Bits


- Assembly programs set architecture (processor) states.
  - Register File
  - Status Flags
  - Memory
  - Program Counter
- Every state is essentially some bits that are stored/loaded.
- Think of the program execution as an FSM.
- The hardware must provide mechanisms to load and store bits.
- There are many different ways to store bits. They have trade-offs.

# Build a 1-Bit Storage

 


- What we would like:
  - D is the data we want to store (0 or 1)
  - C is the control signal
    - When C is 1, Q becomes D (i.e., storing the data)
    - When C is 0, Q doesn't change with D (data stored)

# Bitstable Element

 


# Bitstable Element

 





# Bitstable Element

 


# Bitstable Element

 


# Bitstable Element

 


## Bistable Element

 

# Bitstable Element

 


## Bistable Element

 

$Q+$  *continuously* outputs  $q$ .

# Storing and Accessing 1 Bit



## Bistable Element

 

$q = 0 \text{ or } 1$


# Storing and Accessing 1 Bit

Bistable Element

 
 


# Storing and Accessing 1 Bit

Bistable Element


 


$q = 0 \text{ or } 1$

  


# Storing and Accessing 1 Bit

Bistable Element

  


Setting  $Q+$  to 1

 




# Storing and Accessing 1 Bit



## Bistable Element

 

$q = 0 \text{ or } 1$

 


## Setting $Q+$ to 1

  


# Storing and Accessing 1 Bit


## Bistable Element

 


$q = 0 \text{ or } 1$

 

## Setting $Q+$ to 1

 


## Setting $Q+$ to 0

 


# Storing and Accessing 1 Bit


Bistable Element

 



$q = 0 \text{ or } 1$

 

Setting  $Q+$  to 1

 


Setting  $Q+$  to 0

  


# Storing and Accessing 1 Bit


Bistable Element

 



$q = 0 \text{ or } 1$

 

Setting  $Q+$  to 1

 


Setting  $Q+$  to 0

  


# Storing and Accessing 1 Bit


## Bistable Element

 


$q = 0 \text{ or } 1$

 


## Setting $Q+$ to 1

 

## Setting $Q+$ to 0

 


## $Q+$ value unchanged i.e., stored!

 


# Storing and Accessing 1 Bit


Bistable Element

 


R-S Latch

 


Setting  $Q+$  to 1

 

Setting  $Q+$  to 0

 


$Q+$  value unchanged  
i.e., stored!

 


# Storing and Accessing 1 Bit

Bistable Element

 


$q = 0 \text{ or } 1$


R-S Latch

 


Setting  $Q+$  to 1

 

Setting  $Q+$  to 0

 


$Q+$  value unchanged  
i.e., stored!

 

If  $R$  and  $S$  are different,  $Q+$  is the same as  $S$


# Building on top of R-S Latch

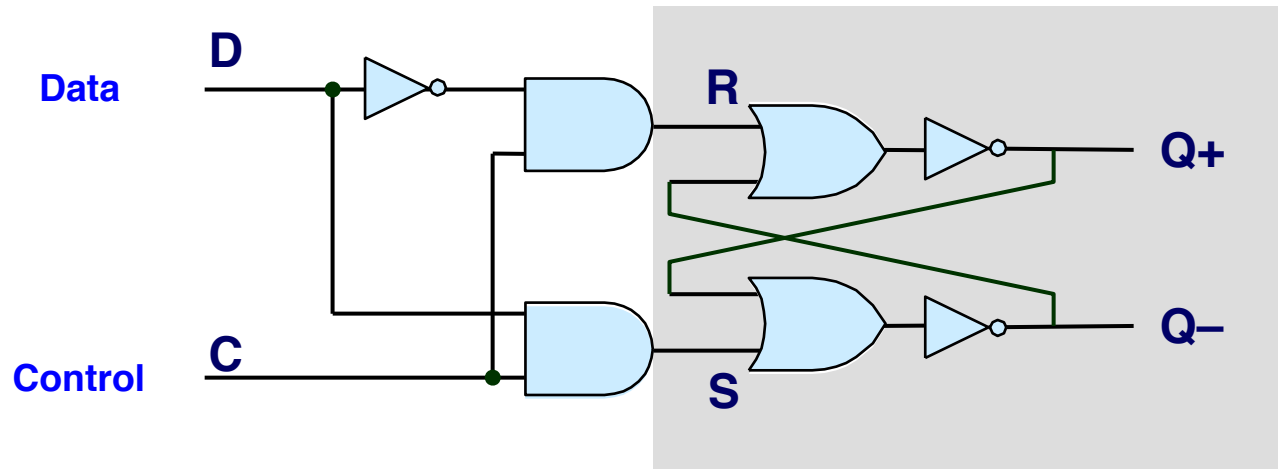


If R and S are different,  $Q+$  is the same as S




# Building on top of R-S Latch

 

 
If R and S are different,  $Q_+$  is the same as S



# Building on top of R-S Latch

 


 If R and S are different, Q+ is the same as S




Q+ will continuously  
change as d changes

# Building on top of R-S Latch

 


If R and S are different, Q+ is the same as S

## Storing Data (Latching)

 


Q+ will continuously change as d changes

# Building on top of R-S Latch

 


**If R and S are different,  $Q_+$  is the same as S**


## Storing Data (Latching)

 

Q+ will continuously change as d changes

 


# Building on top of R-S Latch

 


If R and S are different, Q+ is the same as S

## Storing Data (Latching)

 


Q+ will continuously change as d changes

 


Q+ doesn't change with d

# Building on top of R-S Latch

 


If R and S are different, Q+ is the same as S

**Storing Data (Latching)**

 

Q+ will continuously change as d changes


**Holding Data**

 

Q+ doesn't change with d


# Building on top of R-S Latch

D Latch

 


If R and S are different, Q+ is the same as S

Storing Data (Latching)

 

Q+ will continuously change as d changes


Holding Data

 


Q+ doesn't change with d

# D-Latch is “Transparent”

Latching

 


Changing D

 




# D-Latch is “Transparent”

Latching

 


Changing D

 


# D-Latch is “Transparent”

## Latching

 


## Changing D

 


# D-Latch is “Transparent”

## Latching

 


## Changing D

 


# D-Latch is “Transparent”

## Latching

 


## Changing D

 


# D-Latch is “Transparent”

## Latching

 


## Changing D

 


# D-Latch is “Transparent”

## Latching

 


## Changing D

 


# D-Latch is “Transparent”

## Latching

 


## Changing D

 


- When you want to store **d**, you have to first set **C** to 1, and then set **d**

# D-Latch is “Transparent”

## Latching

 

## Changing D

 


- When you want to store **d**, you have to first set **C** to 1, and then set **d**
- There is a propagation delay of the combinational circuit from **D** to **Q+**. So hold C for a while until the signal is fully propagated




# D-Latch is “Transparent”

## Latching

 


## Changing D

 


- When you want to store **d**, you have to first set **C** to 1, and then set **d**
- There is a propagation delay of the combinational circuit from **D** to **Q+**. So hold **C** for a while until the signal is fully propagated
- Then set **C** to 0. Value latched depends on value of **D** as **C** goes to 0

# D-Latch is “Transparent”

## Latching

 


## Changing D

 


- When you want to store **d**, you have to first set **C** to 1, and then set **d**
- There is a propagation delay of the combinational circuit from **D** to **Q+**. So hold **C** for a while until the signal is fully propagated
- Then set **C** to 0. Value latched depends on value of **D** as **C** goes to 0
- D-latch is *transparent* when **C** is 1

# D-Latch is “Transparent”

## Latching

 


## Changing D

 


- When you want to store **d**, you have to first set **C** to 1, and then set **d**
- There is a propagation delay of the combinational circuit from **D** to **Q+**. So hold **C** for a while until the signal is fully propagated
- Then set **C** to 0. Value latched depends on value of **D** as **C** goes to 0
- D-latch is *transparent* when **C** is 1
- D-latch is “*level-triggered*” b/c **Q** changes as the *voltage level* of **C** rises.


# Edge-Triggered Latch (Flip-Flop)

 


# Edge-Triggered Latch (Flip-Flop)

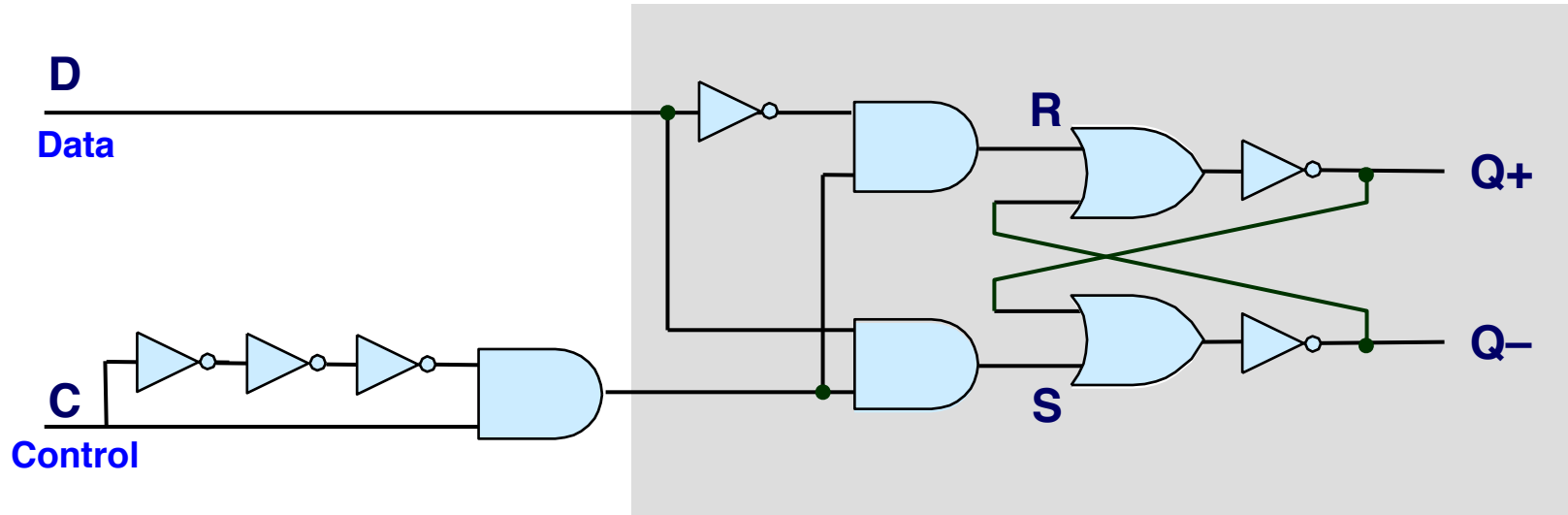


# Edge-Triggered Latch (Flip-Flop)

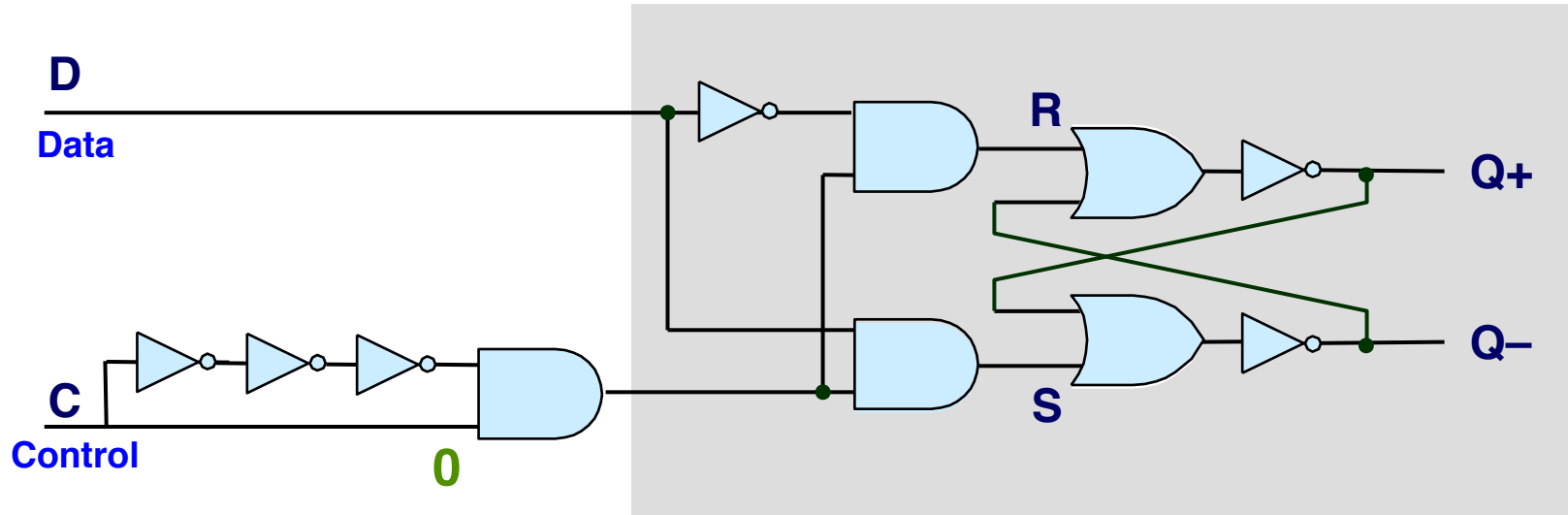

# Edge-Triggered Latch (Flip-Flop)

 


# Edge-Triggered Latch (Flip-Flop)

 





# Edge-Triggered Latch (Flip-Flop)

 


# Edge-Triggered Latch (Flip-Flop)

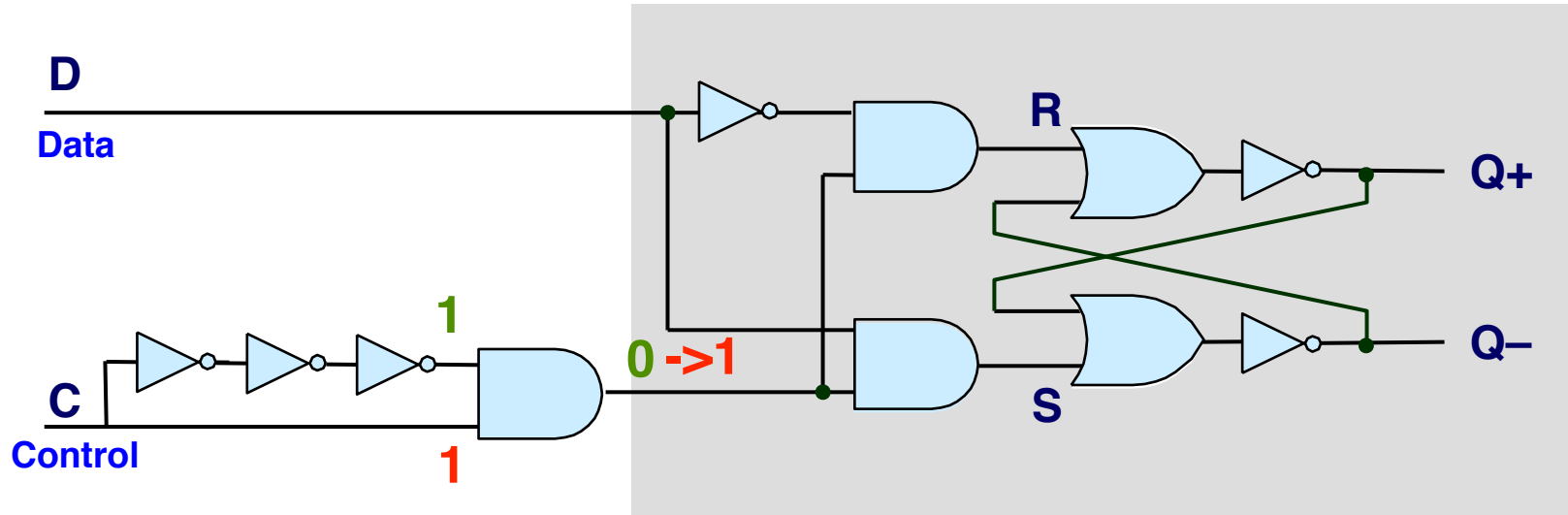



# Edge-Triggered Latch (Flip-Flop)

 



# Edge-Triggered Latch (Flip-Flop)

 

# Edge-Triggered Latch (Flip-Flop)

 
 


# Edge-Triggered Latch (Flip-Flop)

  



- Flip-flop: Only latches data for a brief period

# Edge-Triggered Latch (Flip-Flop)

  

- Flip-flop: Only latches data for a brief period
- Value latched depends on data as **C rises** (i.e., 0→1); usually called at the **rising edge** of **C**


# Edge-Triggered Latch (Flip-Flop)

  


- Flip-flop: Only latches data for a brief period
- Value latched depends on data as **C rises** (i.e., 0→1); usually called at the **rising edge** of **C**
- Output remains stable at all other times




# Why Use a Flip-Flop?

 

 - Because the data we want to store might be temporarily changing before it settles down (due to glitch). We want to capture only the final value.
- If we had a transparent D latch, the latched value would change with F, i.e., temporal glitches will be temporarily stored as well.
- With a flip flop, we can store data only when its value settles: raise the control signal of the flop when F settles.





# Registers

 


- Stores several bits of data
- Collection of edge-triggered latches (D Flip-flops)
- Loads input on rising edge of the C signal

# Registers

  


- Stores several bits of data
- Collection of edge-triggered latches (D Flip-flops)
- Loads input on rising edge of the C signal


# Register Operation

 


# Register Operation

 

# Register Operation

 


# Register Operation

 

- Stores data bits
- For most of time acts as barrier between input and output
- As  $C$  rises, loads input
- So you'd better compute the input before the  $C$  signal rises if you want to store the input data to the register

# Register Operation

 


Output **continuously** produces y after the rising edge unless you cut off power.

- Stores data bits
- For most of time acts as barrier between input and output
- As C rises, loads input
- So you'd better compute the input before the C signal rises if you want to store the input data to the register




# Clock Signal

 

- A special C: periodically oscillating between 0 and 1
- That's called the **clock** signal. Generated by a crystal oscillator inside your computer.


# Clock Signal

 


- A special C: periodically oscillating between 0 and 1
- That's called the **clock** signal. Generated by a crystal oscillator inside your computer.




# Clock Signal

 

 
- A special  $C$ : periodically oscillating between 0 and 1
- That's called the **clock** signal. Generated by a crystal oscillator inside your computer.



# Clock Signal

 


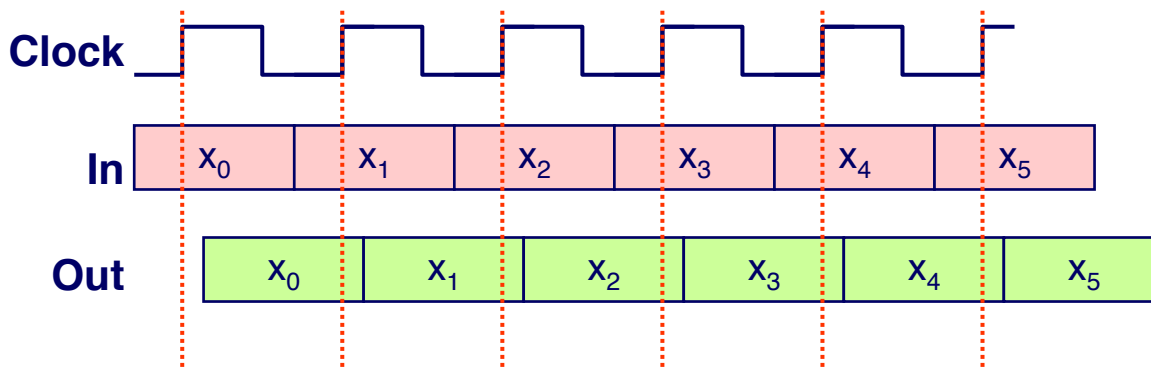- A special C: periodically oscillating between 0 and 1
- That's called the **clock** signal. Generated by a crystal oscillator inside your computer.



 
# Clock Signal

- Cycle time of a clock signal: the time duration between two rising edges.



 
# Clock Signal

- Cycle time of a clock signal: the time duration between two rising edges.



 
# Clock Signal

- Cycle time of a clock signal: the time duration between two rising edges.
- Frequency of a clock signal: how many rising (falling) edges in 1 second.


 
# Clock Signal

- Cycle time of a clock signal: the time duration between two rising edges.
- Frequency of a clock signal: how many rising (falling) edges in 1 second.
- 1 GHz CPU means the clock frequency is 1 GHz





# Clock Signal

- Cycle time of a clock signal: the time duration between two rising edges.
- Frequency of a clock signal: how many rising (falling) edges in 1 second.
- 1 GHz CPU means the clock frequency is 1 GHz
  - The cycle time is  $1/10^9 = 1 \text{ ns}$

