

# **CSC 252: Computer Organization**

## **Spring 2025: Lecture 12**

Instructor: Yuhao Zhu

Department of Computer Science  
University of Rochester

# Announcement

- Programming assignment 3 out.
- See blackboard announcement for PA 1 grades
- Open-book mid-term on Friday at this time
  - Anything on paper is fair, nothing electronically.
- **“I don’t know” is given 15% partial credit**
  - You need to decide if guessing is worthwhile
  - Saves grading time
  - You have to write “I don’t know” and cross out /erase anything else to get credit: A blank answer doesn’t count

# Move Instructions

Byte	0	1	2	3	4	5	6	7	8	9
halt	0	0								
nop	1	0								
cmovXX rA, rB	2	fn	rA	rB						
irmovq V, rB	3	0	F	rB						
rmmovq rA, D(rB)	4	0	rA	rB						
mrmovq D(rB), rA	5	0	rA	rB						
OPq rA, rB	6	fn	rA	rB						
jXX Dest	7	fn								
call Dest	8	0								
ret	9	0								
pushq rA	A	0	rA	F						
popq rA	B	0	rA	F						

The instruction length limits the immediate value and displacement.

irmovq \$0xabcd, %rdx

rmmovq %rsi, 0x41c(%rsp)

mrmovq -12(%rbp), %rcx

# Move Instruction Examples

## Y86-64

```
irmovq $0xabcd, %rdx
```

Encoding: 30 82 cd ab 00 00 00 00 00 00

```
rrmovq %rsp, %rbx
```

Encoding: 20 43

```
mrmovq -12(%rbp), %rcx
```

Encoding: 50 15 f4 ff ff ff ff ff ff ff

```
rmmovq %rsi, 0x41c(%rsp)
```



Encoding: 40 64 1c 04 00 00 00 00 00 00

# Jump/Call Instructions

Byte	0	1	2	3	4	5	6	7	8	9
halt	0	0								
nop	1	0								
cmovXX rA, rB	2	fn	rA	rB						
irmovq V, rB	3	0	F	rB	V					
rmmovq rA, D(rB)	4	0	rA	rB	D					
mrmmovq D(rB), rA	5	0	rA	rB	D					
OPq rA, rB	6	fn	rA	rB						
jXX Dest	7	fn			jle .L4	ally the target address)				
call Dest	8	0	Dest		call foo	e start address of the callee)				
ret	9	0								
pushq rA	A	0	rA	F						
popq rA	B	0	rA	F						


The assembler would assume a start address of the program, and then calculates the address of each instruction.

# How Does An Assembler Work?

  
 
# How Does An Assembler Work?

- The assembler is a program that translates assembly code to binary code
- The OS tells the assembler the start address of the code (sort of...)
- Translate the assembly program line by line
- Need to build a “label map” that maps each label to its address



# Jump Instructions

## Jump Unconditionally

**jmp Dest**    7   0    Dest

## Jump When Less or Equal

**jle Dest**    7   1    Dest

## Jump When Less

**jl Dest**    7   2    Dest

## Jump When Equal

**je Dest**    7   3    Dest

## Jump When Not Equal

**jne Dest**    7   4    Dest

## Jump When Greater or Equal

**jge Dest**    7   5    Dest

## Jump When Greater

**jg Dest**    7   6    Dest



# Subroutine Call and Return

**call Dest**

8

0

Dest

- Push address of next instruction onto stack
- Start executing instructions at Dest
- Like x86-64


**ret**

9

0

- Pop value from stack
- Use as address for next instruction
- Like x86-64


# One More Complication...

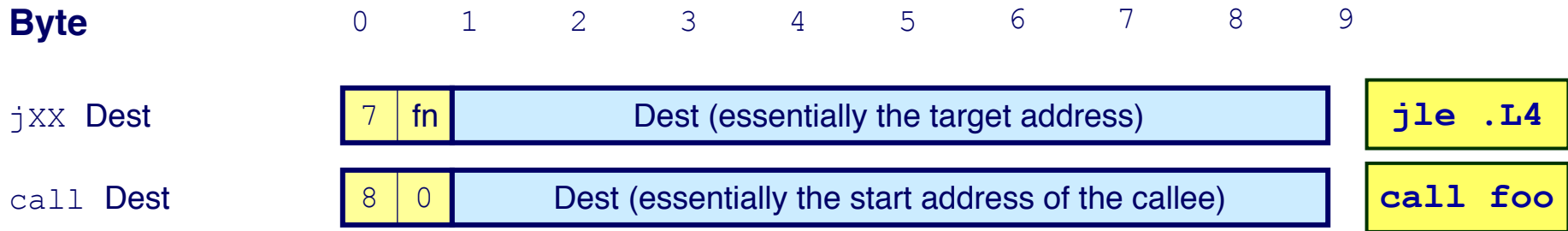

- The instruction length limits how far you can jump/call functions. What if the jump target has a very long address that can't fit in 8 bytes?
  - Or if we can use only say 4 bytes for the target address?
- One alternative: use a super long instruction encoding format.
  - Simple to encode, but space inefficient (waste bits for jumps to short addr.)
- Another alternative: encode the relative address, not the absolute address
  - E.g., encode (.L4 - current address) in Dest
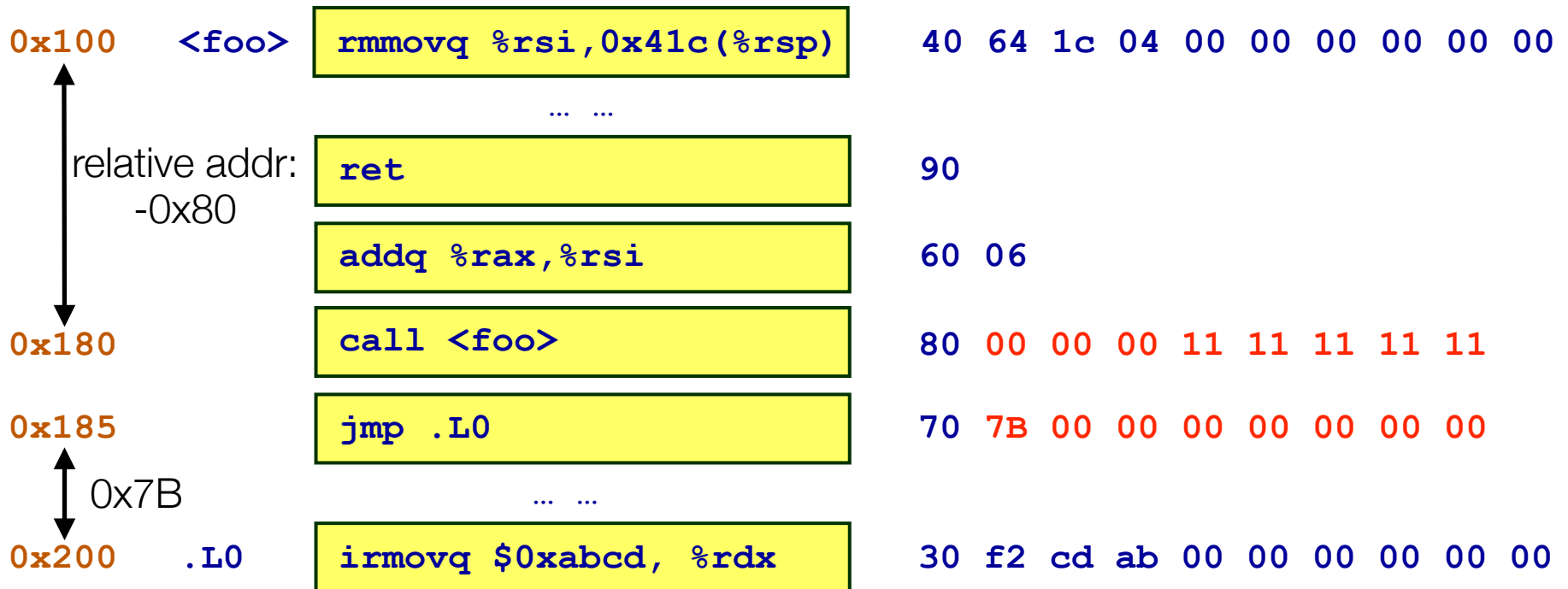
# Using Relative Addresses for Jumps

- What if the ISA encoding uses relative address for jump and call?
- If we use relative address, the exact start address of the code doesn't matter. Why?
- This code is called Position-Independent Code (PIC)



# Miscellaneous Instructions



- Don't do anything




- Stop executing instructions
- Usually can't be executed in the user mode, only by the OS
- Encoding ensures that program hitting memory initialized to zero will halt

# Variable Length Instructions

- X86 (and Y86) is a variable length ISA (1 to 15 bytes), where different instructions have different lengths.
- There are fixed length ISAs: all instructions have the same length
  - ARM's ISA for micro-controllers have a 4-bit ISA. Very Long Instruction Word (VLIW) ISAs have instructions that are hundreds of bytes long.
  - Or you can have a combination of both: e.g., 16-bit ISA with 32-bit extensions (e.g, ARM Thumb-extension).
- Advantages of variable length ISAs
  - More compact. Some instructions do not need that many bits. (Actually what's the optimal way of encoding instructions in a variable length ISA?)
  - Can have arbitrary number of instructions: easy to add new inst.
- What is the down side?
  - Fetch and decode are harder to implement. More on this later.
- A good writeup showing some of the complexity involved:  
<http://www.c-jump.com/CIS77/CPU/x86/lecture.html>

# So far in 252...

 


# Today: Circuits Basics

- Basics
- Circuits for computations
- Circuits for storing data
 
# Overview of Circuit-Level Design

- Fundamental Hardware Requirements
  - Communication: How to get values from one place to another. Mainly three electrical **wires**.
  - Computation: **transistors**. Combinational logic.
  - Storage: **transistors**. Sequential logic.
- Circuit design is often abstracted as **logic design**








# Today: Circuits Basics

- Transistors
- Circuits for computations
- Circuits for storing data



# Inverter (NOT Gate)

 

In	Out
0	1
1	0

  


# NOR Gate (NOT + OR)

  


A	B	C
0	0	1
0	1	0
1	0	0
1	1	0

Note: Serial structure on top, parallel on bottom.


# Basic Logic Gates

 


*NOT*

 


*OR*

 

*NOR*

 


*AND*

 


*NAND*


# Computing with Logic Gates

 

 - Outputs are Boolean functions of inputs
- Respond continuously to changes in inputs **with some small delay**
- **Different gates have different delays (b/c different transistor combinations)**




# Combinational Circuits

 


- A Network of Logic Gates

- Continuously responds to changes on primary inputs
- Primary outputs become (**after some delay**) Boolean functions of primary inputs

# Bit Equality

 


# Delay of Bit Equal Circuit

 

- What's the delay of this bit equal circuit?
  - Assuming 1-input NOT takes 1 unit of time, 2-input AND takes 4.3, and 2-input OR takes 4.7
- The delay of a circuit is determined by its “critical path”
  - The path between an input and the output that the maximum delay
  - Estimating the critical path delay is called static timing analysis




# So far in 252...

 

# Today: Circuits Basics



- Basics
- Circuits for computations
- Circuits for storing data

# Delay of Bit Equal Circuit

 



- What's the delay of this bit equal circuit?
  - Assuming 1-input NOT takes 1 unit of time, 2-input AND takes 4.3, and 2-input OR takes 4.7
- The delay of a circuit is determined by its “critical path”
  - The path between an input and the output that the maximum delay
  - Estimating the critical path delay is called static timing analysis

# Glitch/Hazard

  


- A glitch is an unnecessary signal transition without functionality.
- Why is it bad? When transistors switch they consume power, but the power consumed during a glitch is a waste.
- Without care, glitch power dissipation is 20%-70% of total power dissipation.

# 64-bit Equality

  

 
# Bit-Level Multiplexor (MUX)

- Control signal  $s$
- Data signals  $A$  and  $B$
- Output  $A$  when  $s=1$ ,  $B$  when  $s=0$




```
bool out = (s&&a) || (!s&&b)
```

 
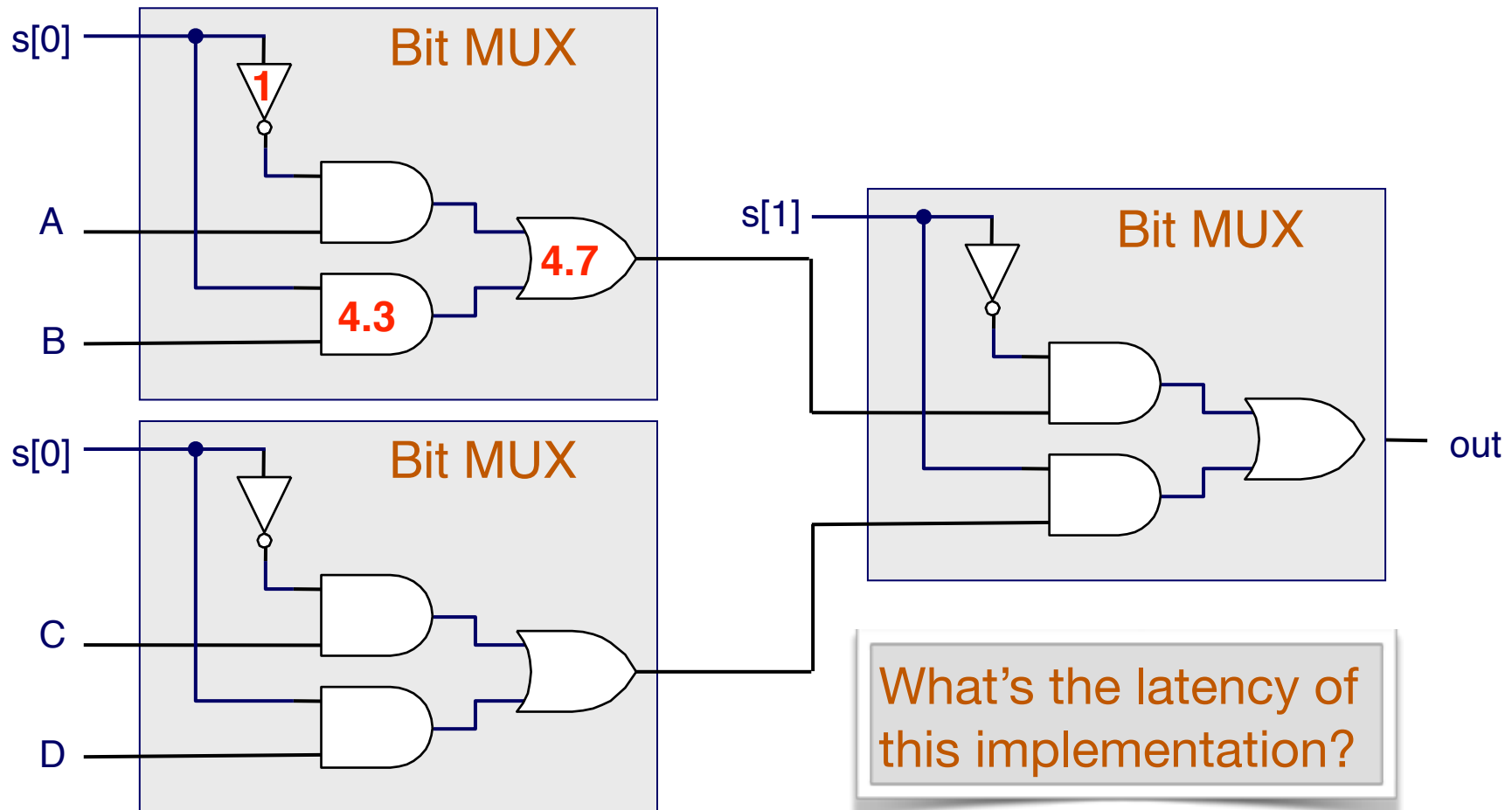
# 4-Input Multiplexor

- Control signal  $s$ ; Data signals A, B, C, and D
- Output: A when  $s = 00$ , B when  $s = 01$ , C when  $s = 10$ , D when  $s = 11$



# Logic Design and VLSI

- The number of inputs of a gate (fan-in) and the number of outputs of a gate (fan-out) will affect the gate delay.
- Think of logic gates as LEGO chips, using which you generate the gate level circuit design for complex functionalities.
- A standard cell library is a collection of well defined and appropriately characterized logic gates (delay, operating voltage, etc.) that can be used to implement a digital design.
- The *logic synthesis tool* will automatically generate the “best” gate-level implementation of a piece of logic.
- Take a Logic Design or Very Large Scale Integrated-Circuit (VLSI) course if you want to know more about circuit design.
  - Logic design uses the gate-level abstractions
  - VLSI tells you how the gates are implemented at transistor-level



# Recall: Full (1-bit) Adder

Add two bits and carry-in,  
produce one-bit sum and carry-out.

$$\begin{aligned} S = & (\sim A \ \& \ \sim B \ \& \ C_{in}) \\ & | (\sim A \ \& \ B \ \& \ \sim C_{in}) \\ & | (A \ \& \ \sim B \ \& \ \sim C_{in}) \\ & | (A \ \& \ B \ \& \ C_{in}) \end{aligned}$$


$$\begin{aligned} C_{ou} = & (\sim A \ \& \ B \ \& \ C_{in}) \\ & | (A \ \& \ \sim B \ \& \ C_{in}) \\ & | (A \ \& \ B \ \& \ \sim C_{in}) \\ & | (A \ \& \ B \ \& \ C_{in}) \end{aligned}$$

A	B	C <sub>in</sub>	S	C <sub>ou</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1
 
# Recall: 1-bit Full Adder


$$C_{ou} = (\sim A \& B \& C_{in}) \mid (A \& \sim B \& C_{in}) \mid (A \& B \& \sim C_{in}) \mid (A \& B \& C_{in})$$

Add two bits and carry-in,  
produce one-bit sum and carry-out.



 
# Recall: Four-bit Adder

- Ripple-carry Adder
  - Simple, but performance linear to bit width
- Carry look-ahead adder (CLA)
  - Generate all carriers simultaneously




# Arithmetic Logic Unit

 

- An ALU performs multiple kinds of computations.
- The actual computation depends on the selection signal  $s$ .
- Also sets the condition codes (status flags)
- For instance:
  - $X + Y$  when  $s == 00$
  - $X - Y$  when  $s == 01$
  - $X \& Y$  when  $s == 10$
  - $X \wedge Y$  when  $s == 11$
- How can this ALU be implemented?
 
# Arithmetic Logic Unit

- Implement 4 different circuits, one for each operation.
- Then use a MUX to select the results




# Today: Circuits Basics

- Transistors
- Circuits for computations
- Circuits for storing data

# The Need for Storing Bits

- Assembly programs set architecture (processor) states.
  - Register File
  - Status Flags
  - Memory
  - Program Counter
- Every state is essentially some bits that are stored/loaded.
- Think of the program execution as an FSM.
- The hardware must provide mechanisms to load and store bits.
- There are many different ways to store bits. They have trade-offs.


# Build a 1-Bit Storage

 


- What we would like:
  - D is the data we want to store (0 or 1)
  - C is the control signal
    - When C is 1, Q becomes D (i.e., storing the data)
    - When C is 0, Q doesn't change with D (data stored)



# Bitstable Element

 


## Bistable Element

 

$Q+$  *continuously* outputs  $q$ .


# Storing and Accessing 1 Bit

Bistable Element

 


$q = 0 \text{ or } 1$


R-S Latch

 


Setting  $Q+$  to 1

 

Setting  $Q+$  to 0

 


$Q+$  value unchanged  
i.e., stored!

 

If  $R$  and  $S$  are different,  $Q+$  is the same as  $S$


# Building on top of R-S Latch

D Latch

 


If R and S are different, Q+ is the same as S

Storing Data (Latching)

 

Q+ will continuously change as d changes

Holding Data

 

Q+ doesn't change with d