

# **CSC 252: Computer Organization**


## **Spring 2024: Lecture 14**

Instructor: Yuhao Zhu

Department of Computer Science  
University of Rochester
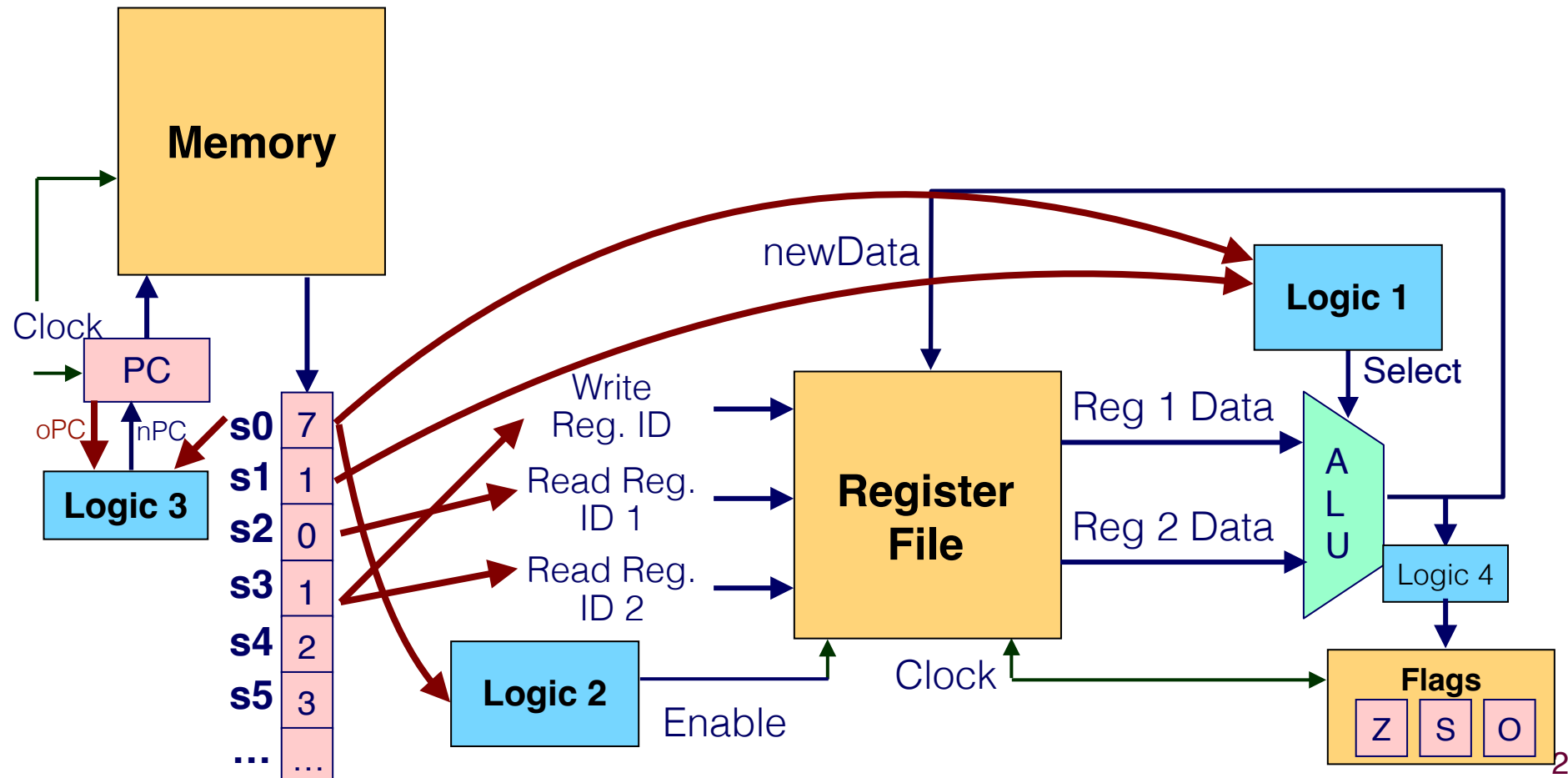
# Executing a JLE instruction

- Logic 1: if (s0 == 6) select = s1;
- Logic 2: if (s0 == 6) Enable = 1; else Enable = 0;



jle Dest

7


1

Dest

# Executing a JLE instruction


- Logic 3??

if (s0 == 6) nPC = oPC + 2;

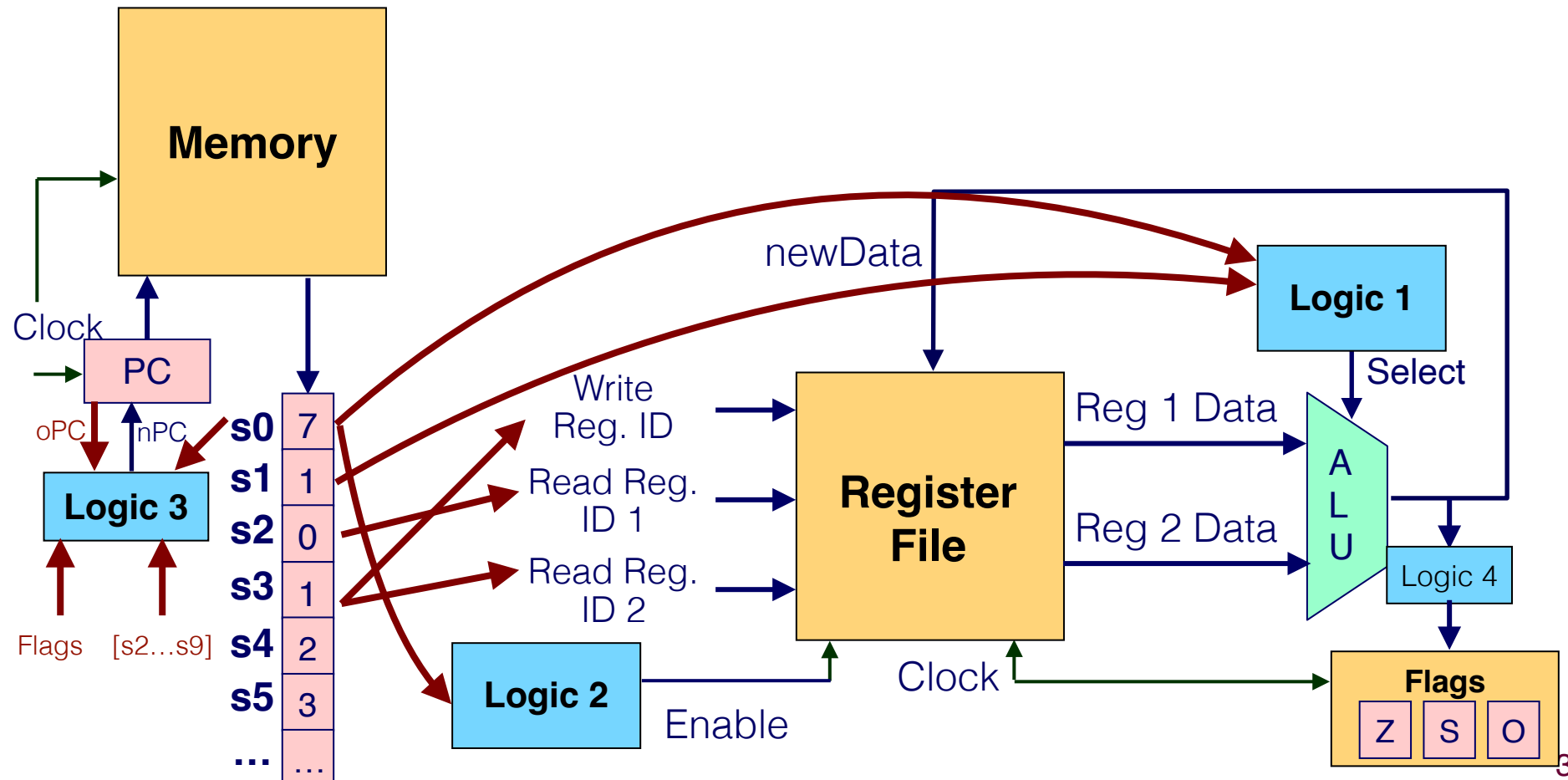

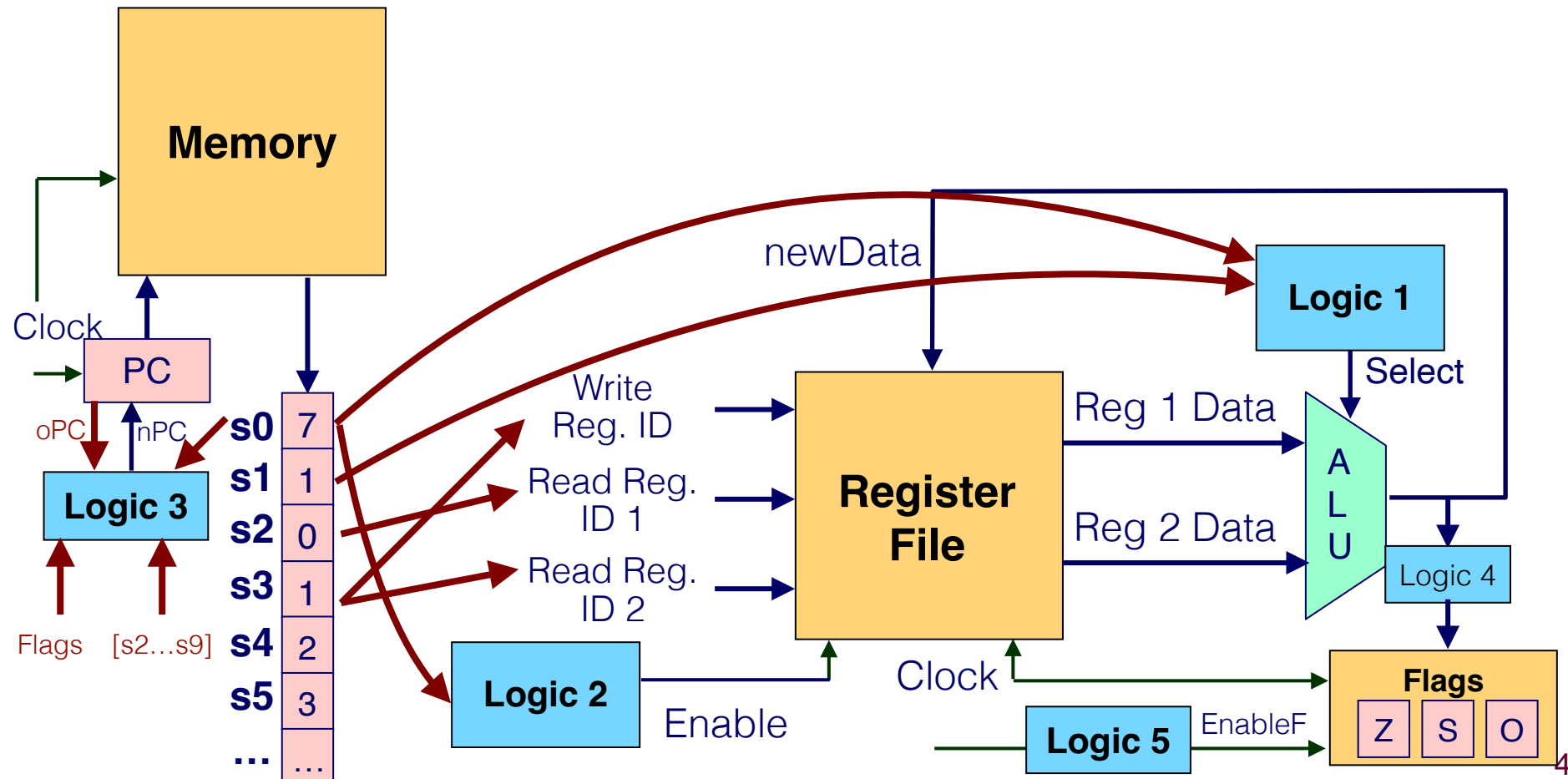
# Executing a JLE instruction

- Logic 4? Does JLE write flags?
- Need another piece of logic.
- Logic 5: if (s0 == 7) EnableF = 0; else if (s0 == 6) EnableF = 1;




# Microarchitecture (So far)

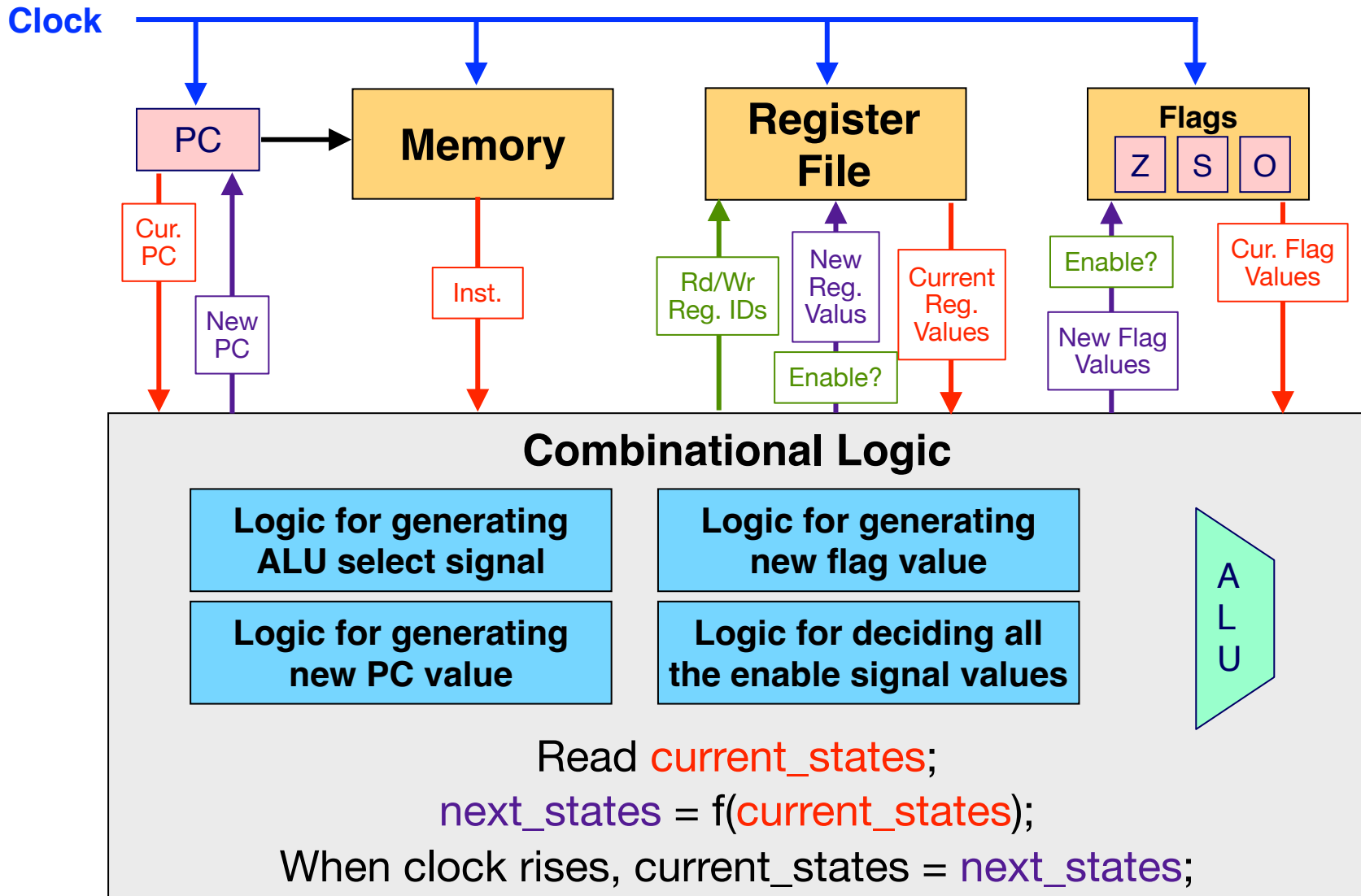
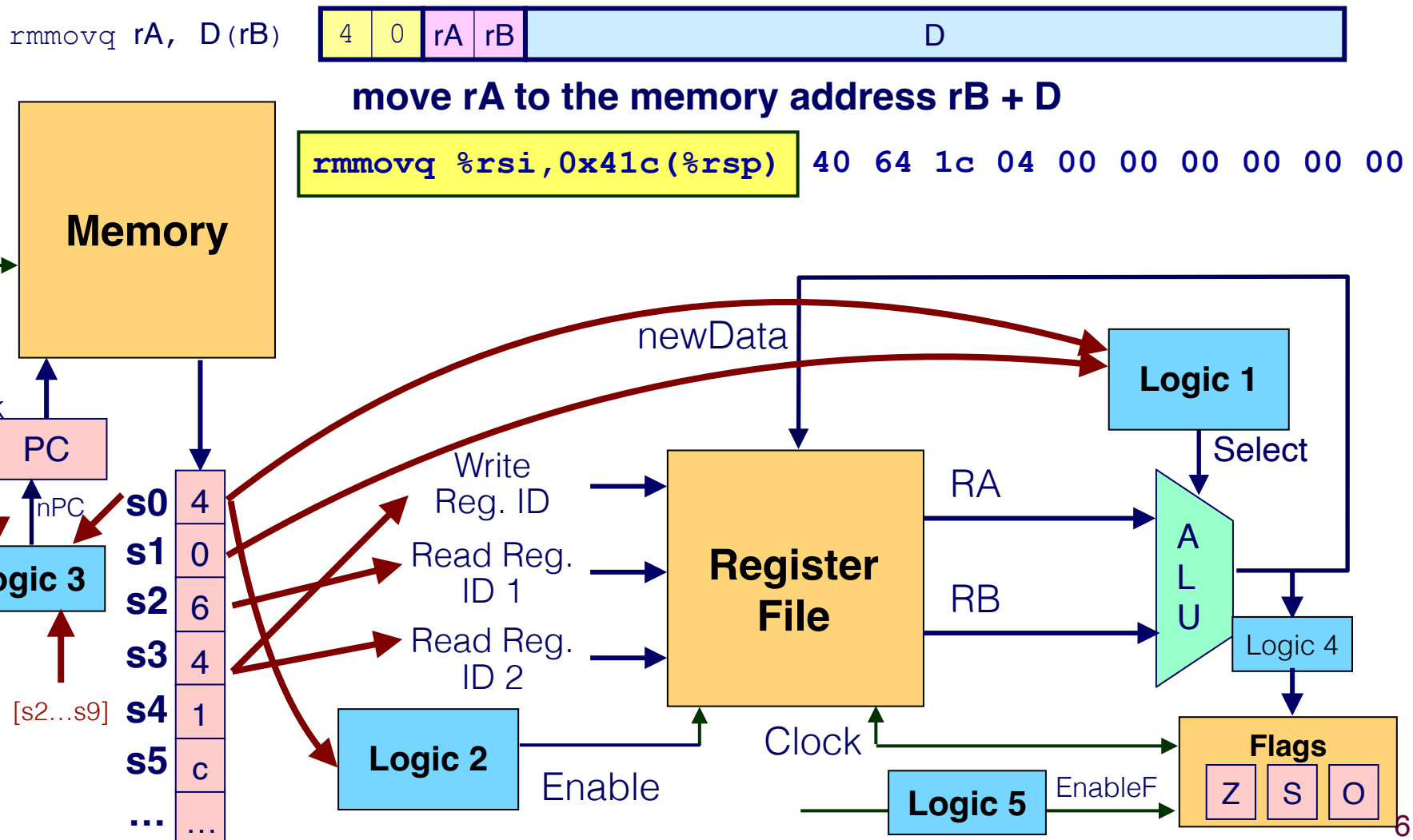
# Executing a MOV instruction

- How do we modify the hardware to execute a move instruction?



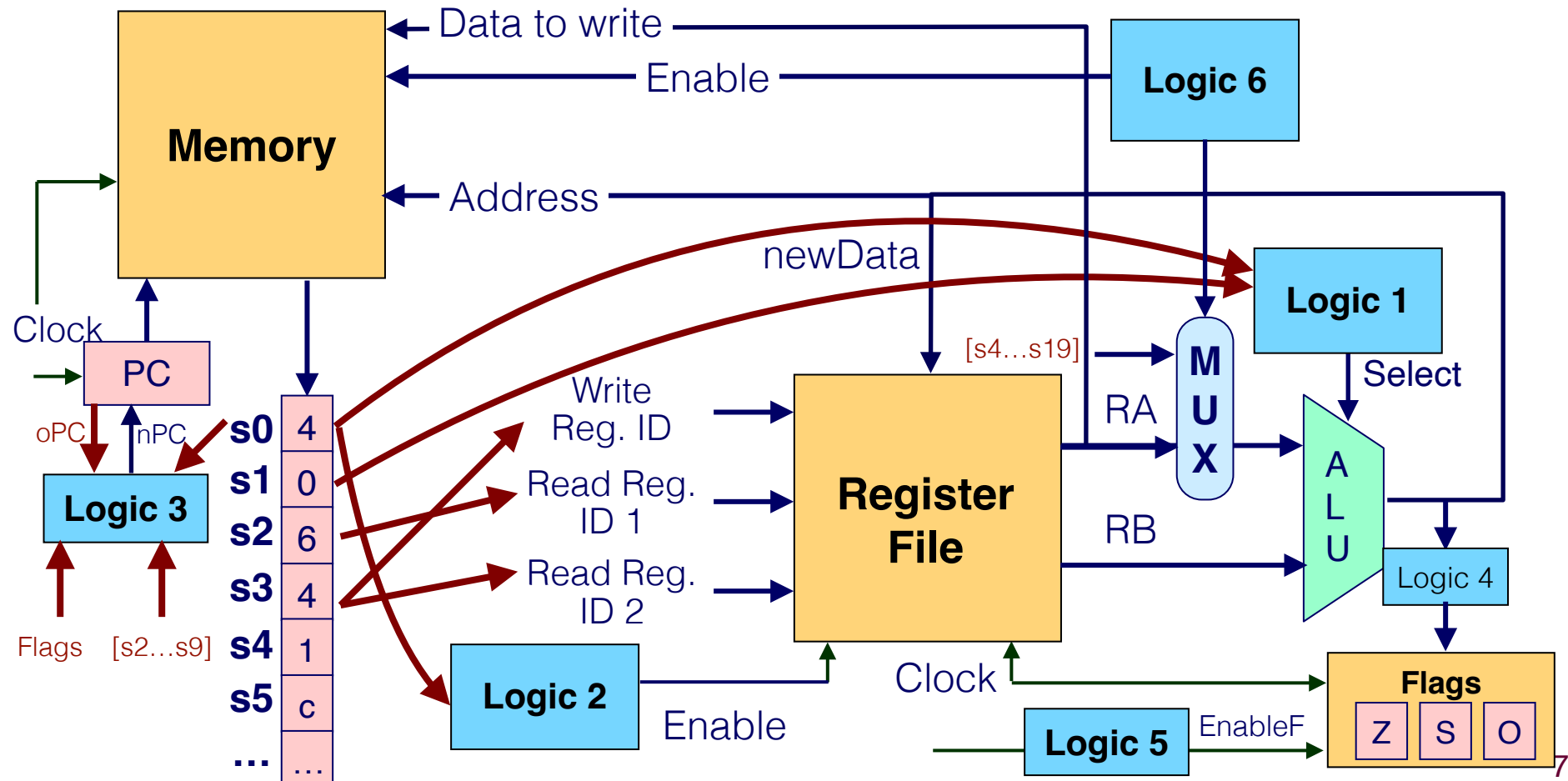
## move rA to the memory address rB + D

rmmovq rA, D(rB)




- Need new logic (Logic 6) to select the input to the ALU for Enable.
- How about other logics?



# How About Memory to Register MOV?

move data at memory address  $rB + D$  to  $rA$

`mrmovq D(rB), rA`

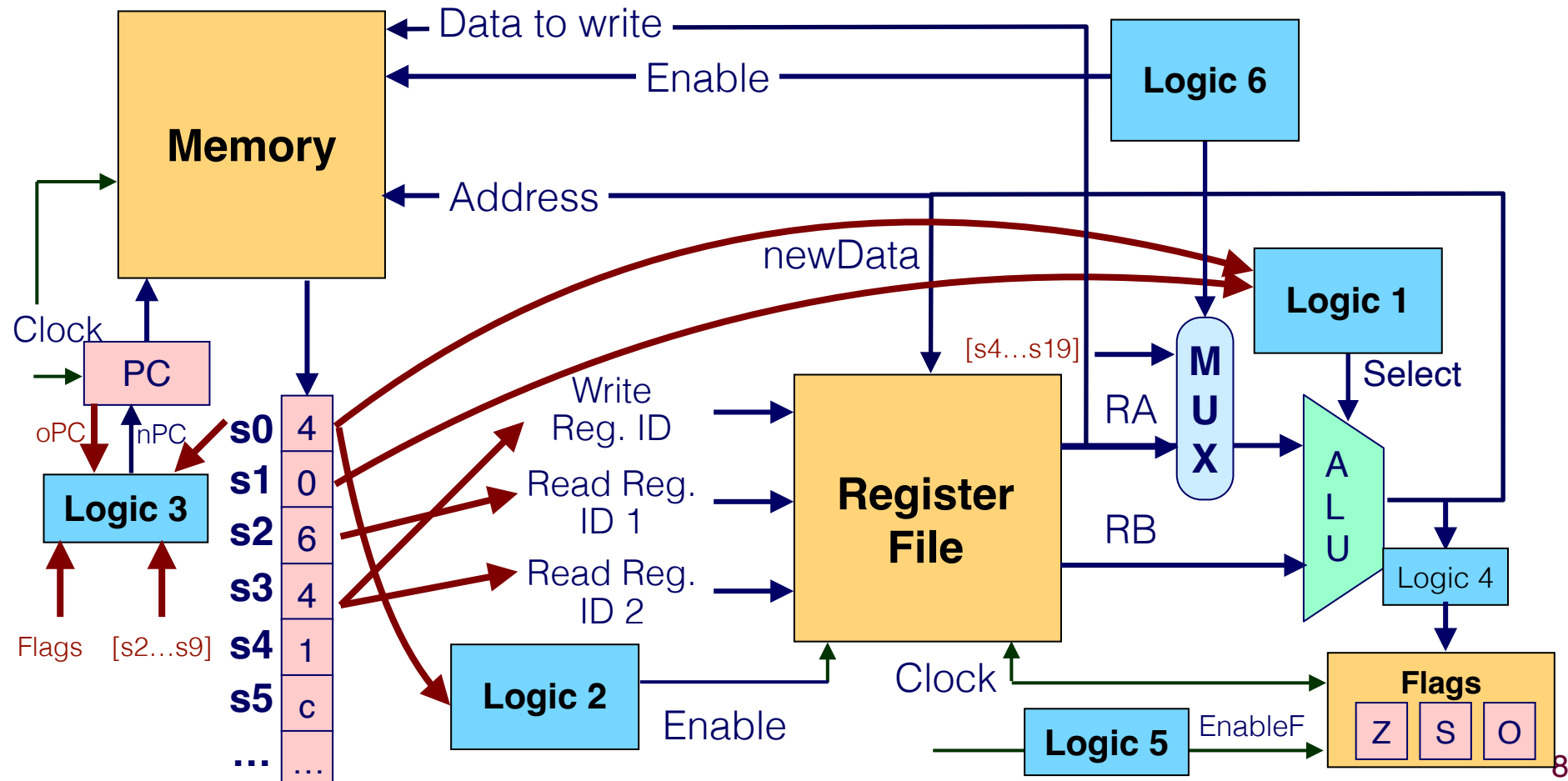





# How About Memory to Register MOV?

move data at memory address  $rB + D$  to  $rA$


`mrmovq D(rB), rA`

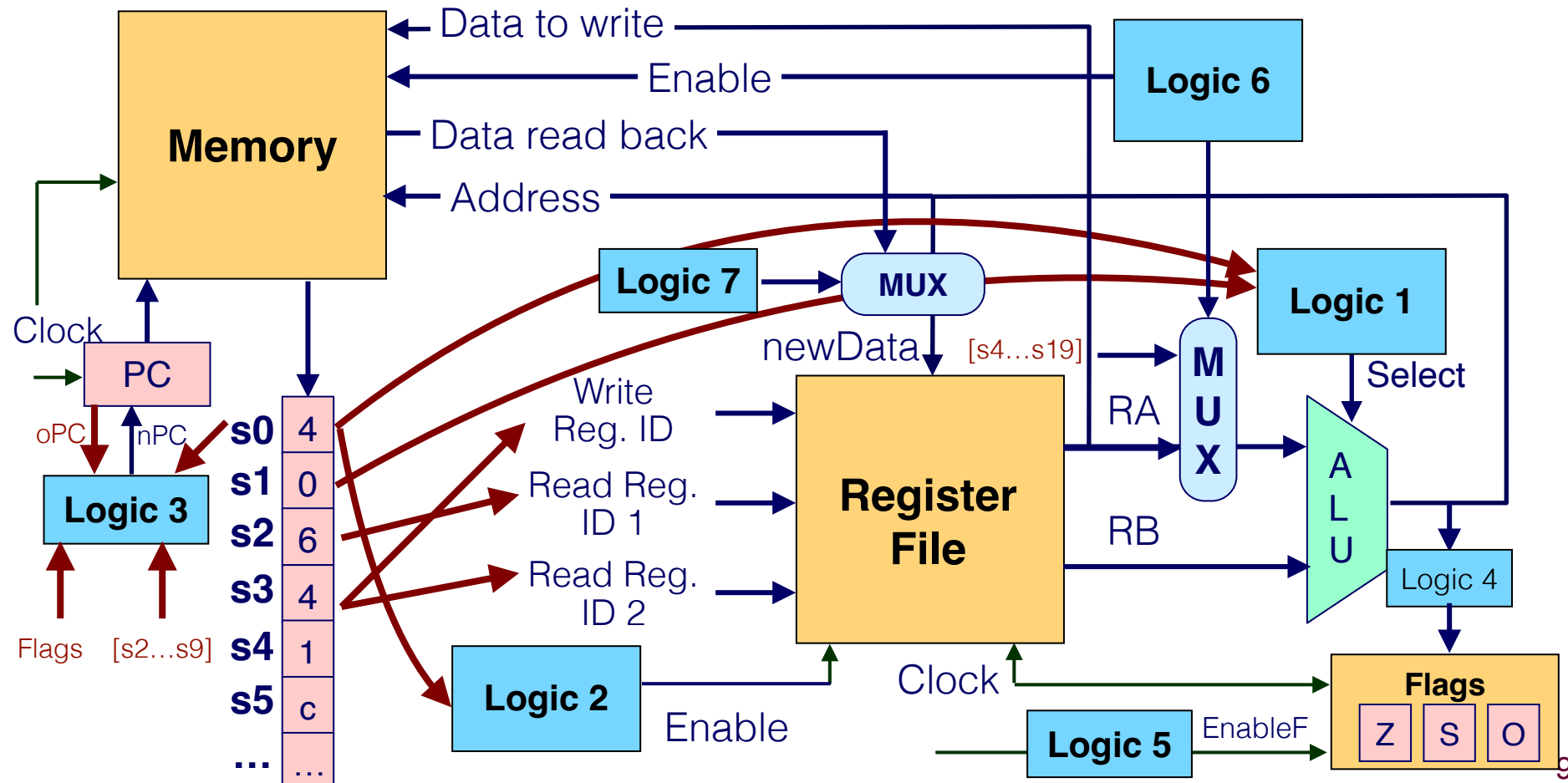

# Microarchitecture (with MOV)

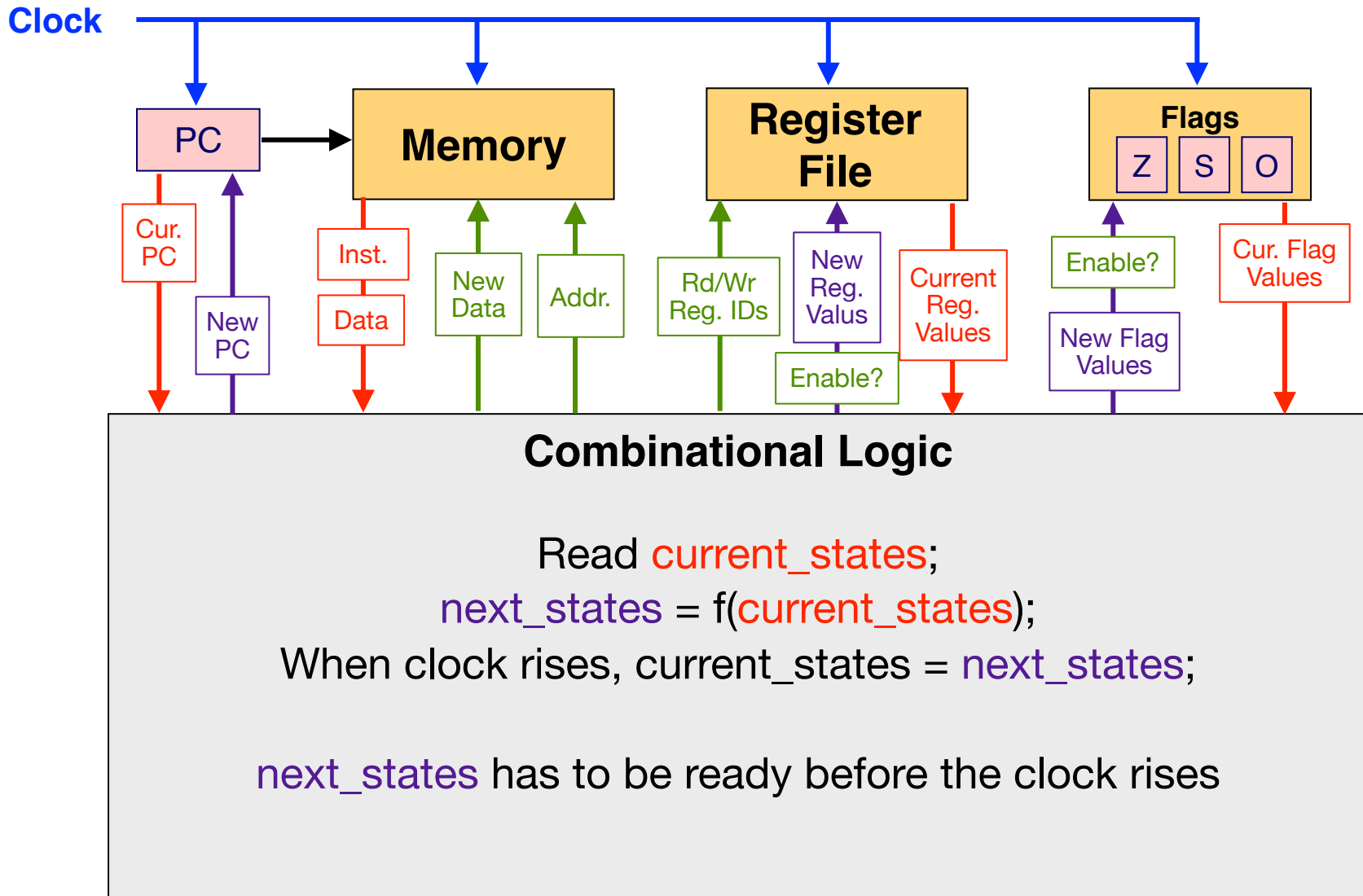

# Single-Cycle Microarchitecture

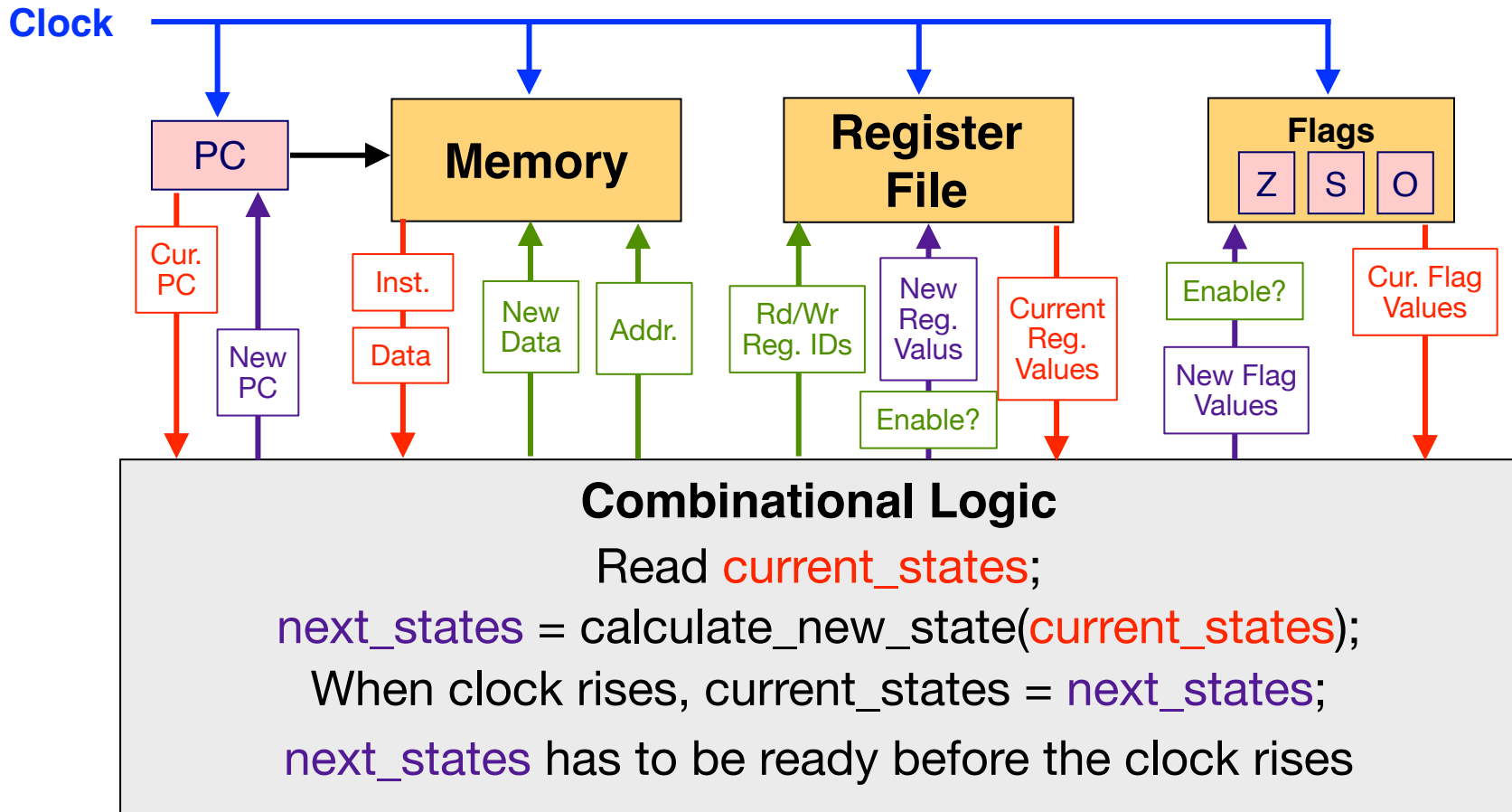

## Key principles:

**States** are stored in storage units, e.g., Flip-flops (and SRAM and DRAM, later..)  
New states are calculated by combination logic.


# Single-Cycle Microarchitecture: Illustration



Think of it as a state machine

Every cycle, one instruction gets executed. At the end of the cycle, architecture states get modified.


States (All updated as clock rises)

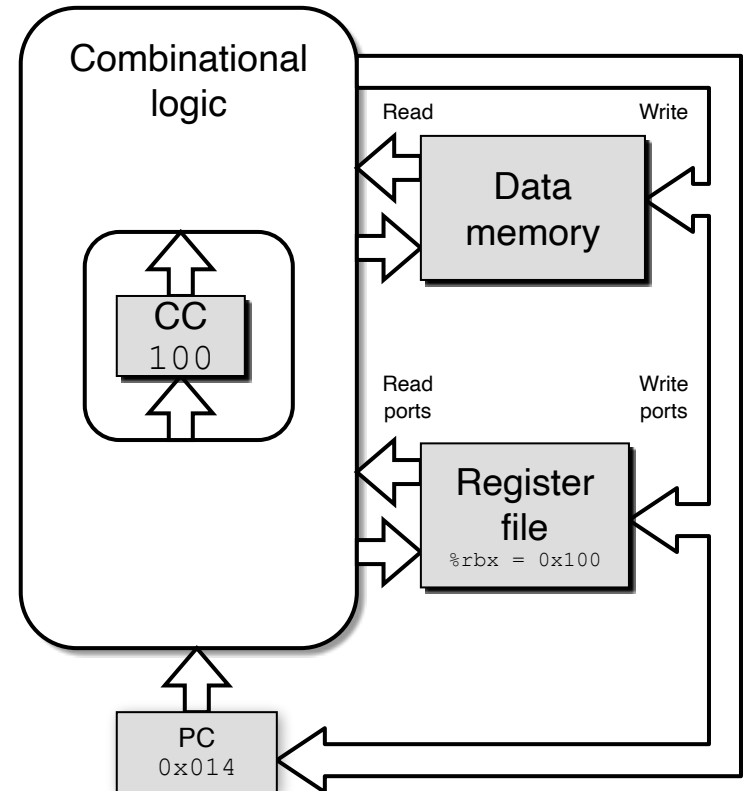- PC register
- Cond. Code register
- Data memory
- Register file




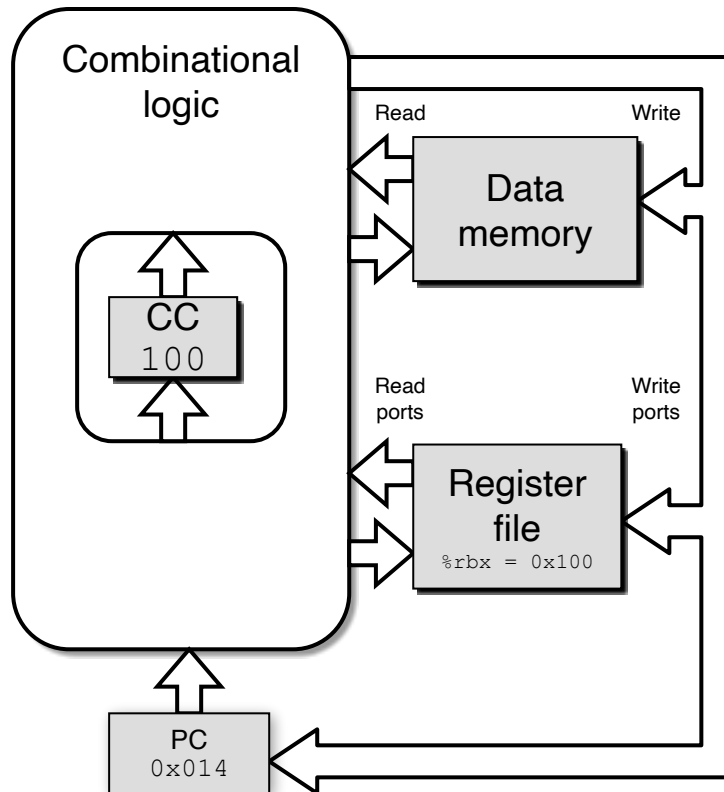 

 
- state set according to second `irmovq` instruction
- combinational logic starting to react to state changes




Cycle 1:	0x000:	<code>irmovq \$0x100,%rbx</code>	# %rbx <-- 0x100
Cycle 2:	0x00a:	<code>irmovq \$0x200,%rdx</code>	# %rdx <-- 0x200
Cycle 3:	0x014:	<code>addq %rdx,%rbx</code>	# %rbx <-- 0x300 CC <-- 000
Cycle 4:	0x016:	<code>je dest</code>	# Not taken
Cycle 5:	0x01f:	<code>rmmovq %rbx,0(%rdx)</code>	# M[0x200] <-- 0x300

 


 
- state set according to second `irmovq` instruction
- combinational logic generates results for `addq` instruction



Cycle 1:	0x000:	irmovq \$0x100,%rbx	# %rbx <-- 0x100
Cycle 2:	0x00a:	irmovq \$0x200,%rdx	# %rdx <-- 0x200
Cycle 3:	0x014:	addq %rdx,%rbx	# %rbx <-- 0x300 CC <-- 000
Cycle 4:	0x016:	je dest	# Not taken
Cycle 5:	0x01f:	rmmovq %rbx,0(%rdx)	# M[0x200] <-- 0x300

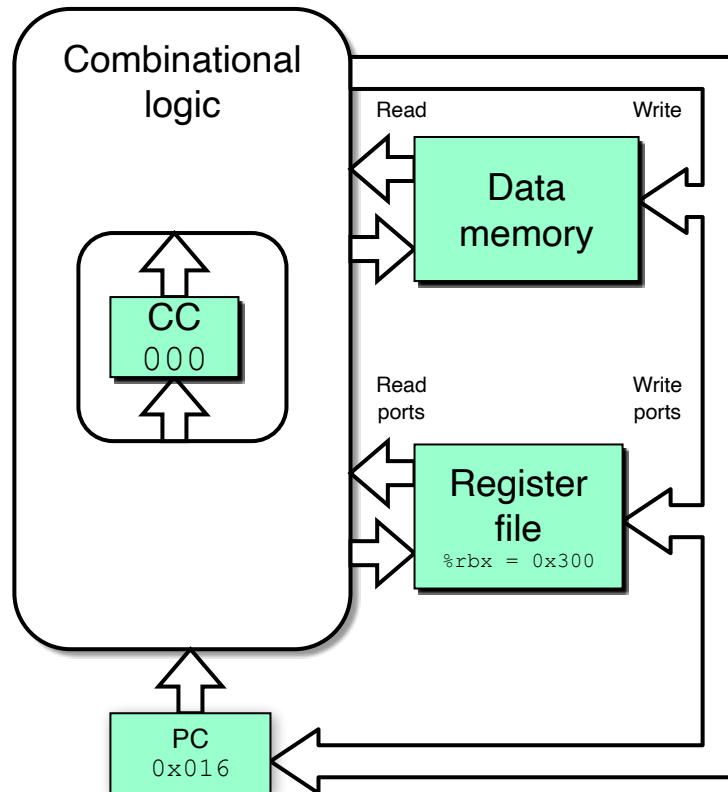

 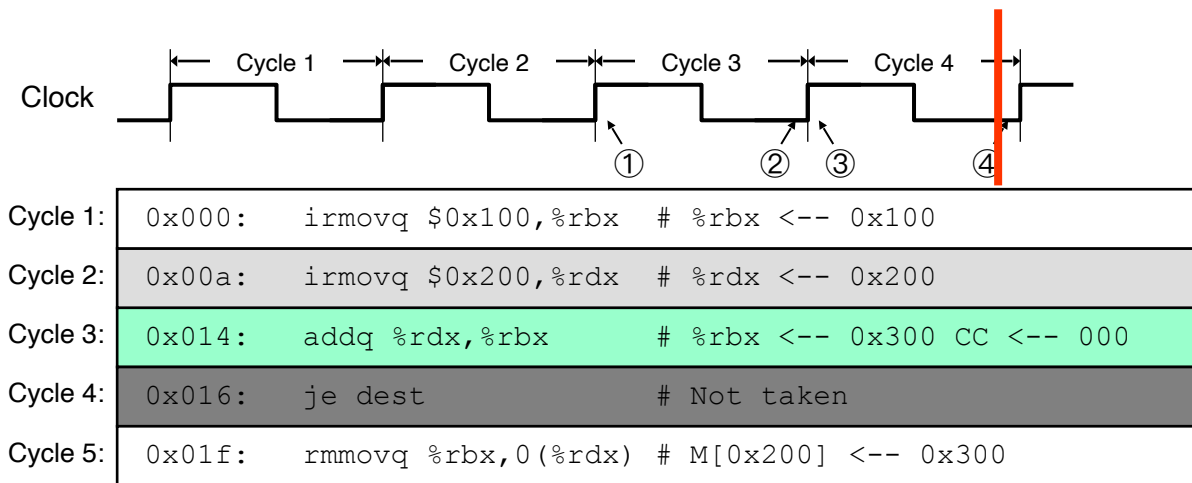- state set according to addq instruction
- combinational logic starting to react to state changes



- state set according to `addq` instruction
- combinational logic generates results for `je` instruction



# Performance Model

$$\begin{aligned} \text{Execution time} &= \text{\# of Dynamic Instructions} && \text{CPI} \\ \text{of a program} &&& \\ \text{(in seconds)} &&& \\ &\times \boxed{\text{\# of cycles taken to execute an instruction (on average)}} && \\ &/ \boxed{\text{number of cycles per second}} && \text{Clock Frequency} \\ &&& \text{(1/cycle time)} \end{aligned}$$

# Improving Performance

Execution time  
of a program  
(in seconds) = # of Dynamic Instructions

X # of cycles taken to execute an instruction (on average)


/ number of cycles per second

- 1. Reduce the total number of instructions executed (mainly done by the compiler and/or programmer).
- 2. Increase the clock frequency (reduce the cycle time). Has huge power implications.
- 3. Reduce the CPI, i.e., execute more instructions in one cycle.
- We will talk about one technique that simultaneously achieves 2 & 3.

# Limitations of a Single-Cycle CPU

- Cycle time
  - Every instruction finishes in one cycle.
  - The absolute time takes to execute each instruction varies. Consider for instance an ADD instruction and a JMP instruction.
  - But the cycle time is uniform across instructions, so the cycle time needs to accommodate the worst case, i.e., the slowest instruction.
  - How do we shorten the cycle time (increase the frequency)?
- CPI
  - The entire hardware is occupied to execute one instruction at a time. Can't execute multiple instructions at the same time.
  - How do execute multiple instructions in one cycle?


# A Motivating Example

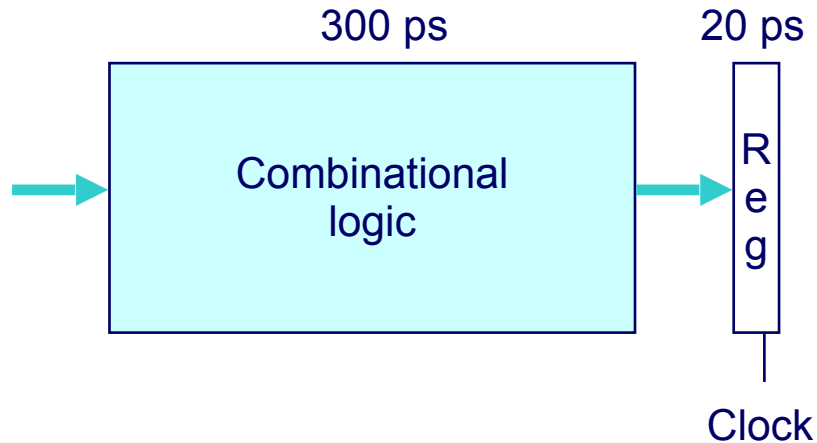

- Computation requires total of 300 picoseconds
- Additional 20 picoseconds to save result in register
- Must have clock cycle time of at least 320 ps

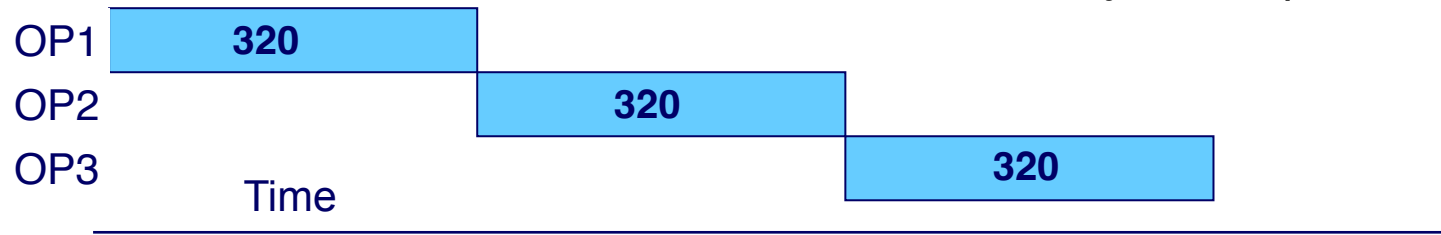
# Pipeline Diagrams

- Time to finish 3 insts = 960 ps
- Each inst.'s latency is 320 ps




- 3 instructions will take 960 ps to finish
  - First cycle: Inst 1 takes 300 ps to compute new state, 20 ps to store the new states
  - Second cycle: Inst 2 starts; it takes 300 ps to compute new states, 20 ps to store new states
  - And so on...

# 3-Stage Pipelined Version

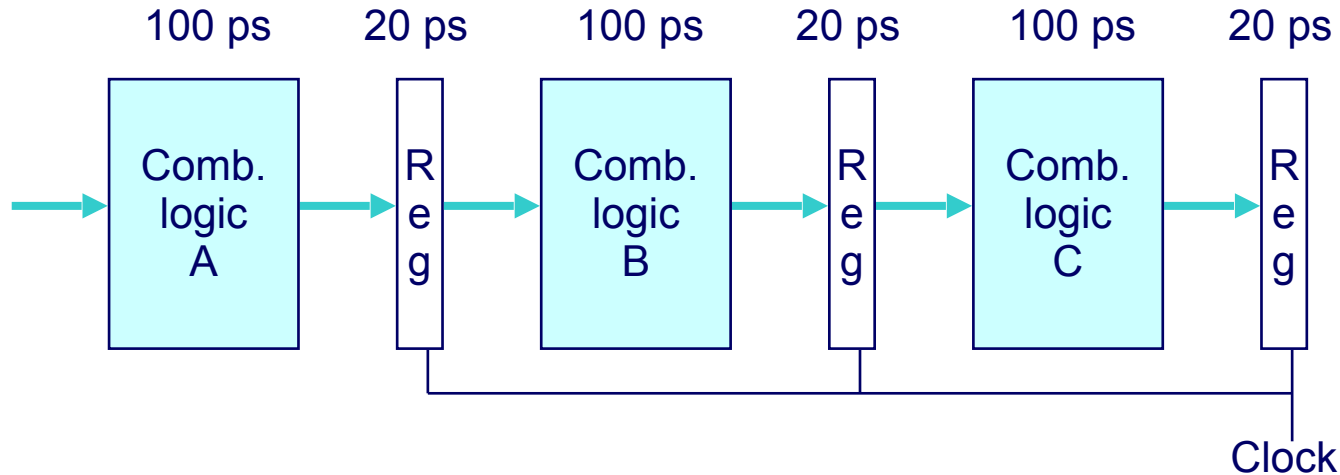


- Divide combinational logic into 3 stages of 100 ps each
- Insert registers between stages to store intermediate data between stages. These are call pipeline registers (ISA-invisible)
- Can begin a new instruction as soon as the previous one finishes stage A and has stored the intermediate data.
  - Begin new operation every **120 ps**
  - **Cycle time can be reduced to 120 ps**

# 3-Stage Pipelined Version

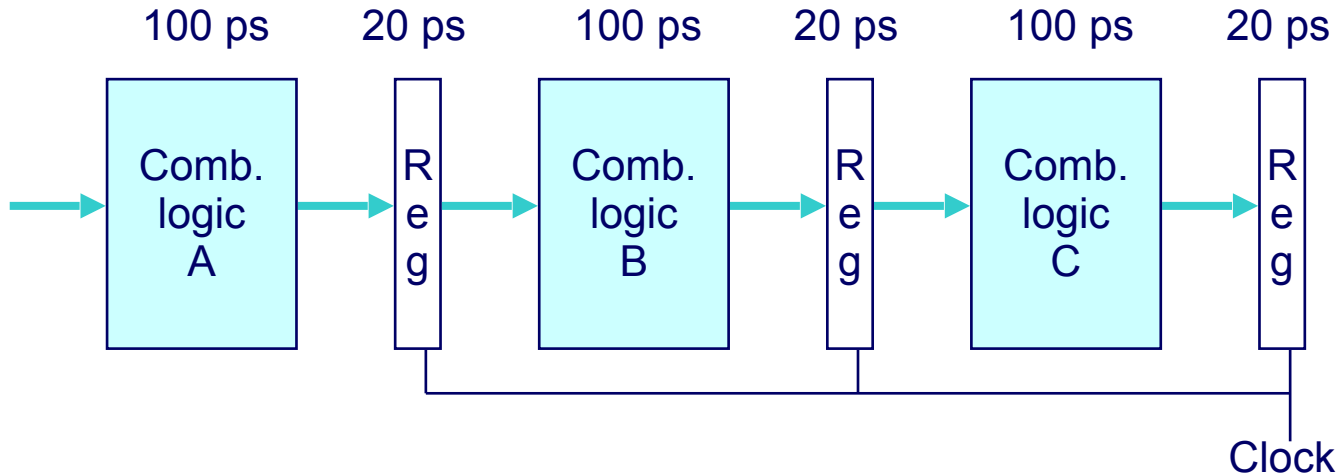


## 3-Stage Pipelined

 


# Comparison

## Unpipelined

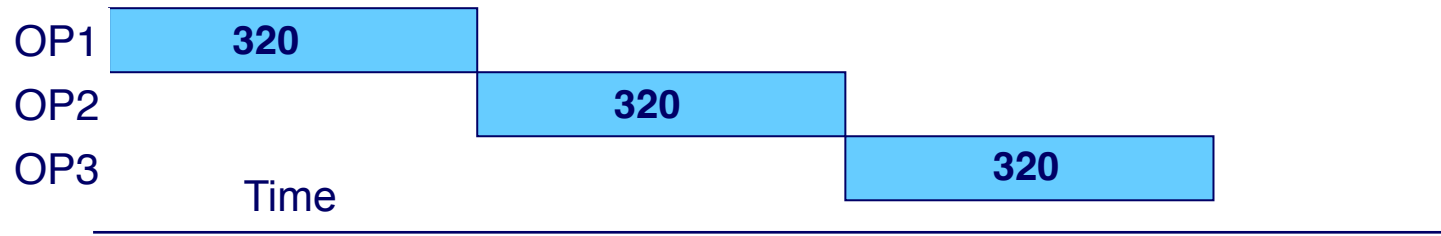

- Time to finish 3 insts = 960 ps
- Each inst.'s latency is 320 ps

## 3-Stage Pipelined

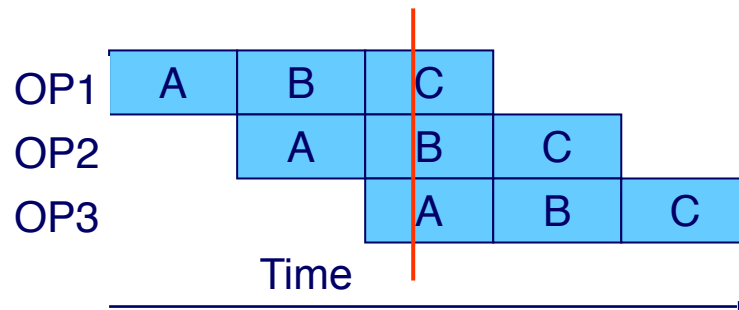


- Time to finish 3 insets =  $120 * 5 = 600$  ps
- But each inst.'s latency increases:  $120 * 3 = 360$  ps



 
# Benefits of Pipelining

- Time to finish 3 insts = 960 ps
- Each inst.'s latency is 320 ps



**1. Reduce the cycle time from 320 ps to 120 ps**

 
**2. CPI reduces from 1 to 1/3 (i.e., executing 3 instructions in one cycle)**



- Time to finish 3 insts =  $120 \times 5 = 600$  ps
- But each inst.'s latency increases:  $120 \times 3 = 360$  ps

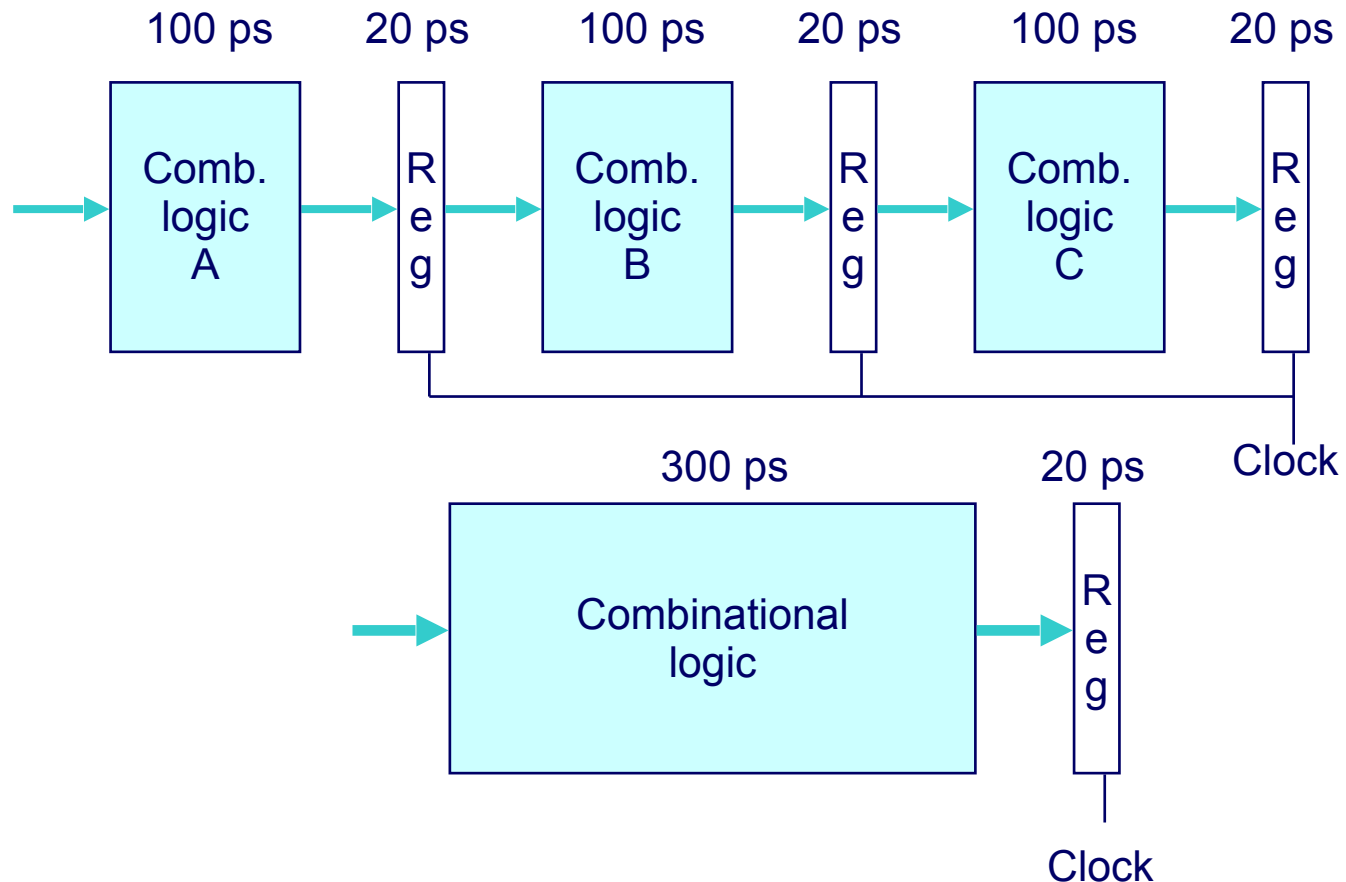
# Pipeline Trade-offs

- Pros: Decrease the total execution time (Increase the “**throughput**”).
- Cons: Increase the latency of each instruction as new registers are needed between pipeline stages.



 
# Throughput

- The rate at which the processor can finish executing an instruction (at the steady state).


 
# One Requirement of Pipelining



- The stages need to be using different hardware structures.
- That is, Stage A, Stage B, and Stage C need to exercise different parts of the combination logic.



- Time to finish 3 insets =  $120 * 5 = 600$  ps
- But each inst.'s latency increases:  $120 * 3 = 360$  ps

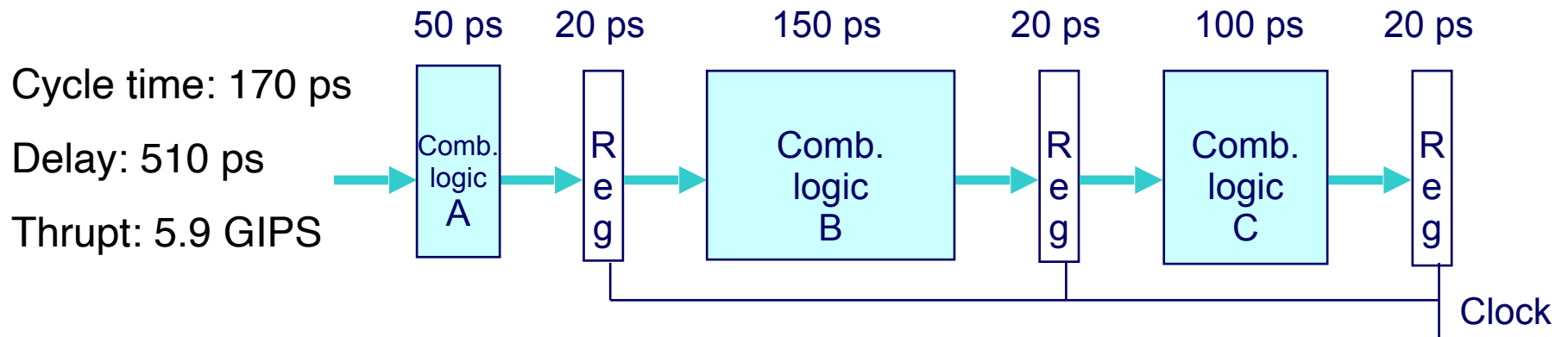
 
# Aside: Unbalanced Pipeline

- A pipeline's delay is limited by the slowest stage. This limits the cycle time and the throughput



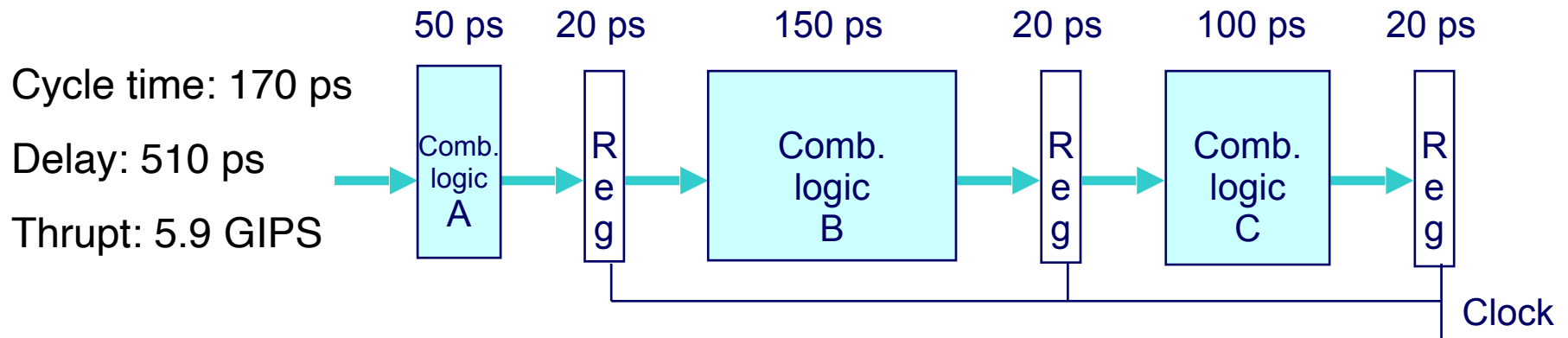 
# Aside: Unbalanced Pipeline

- A pipeline's delay is limited by the slowest stage. This limits the cycle time and the throughput


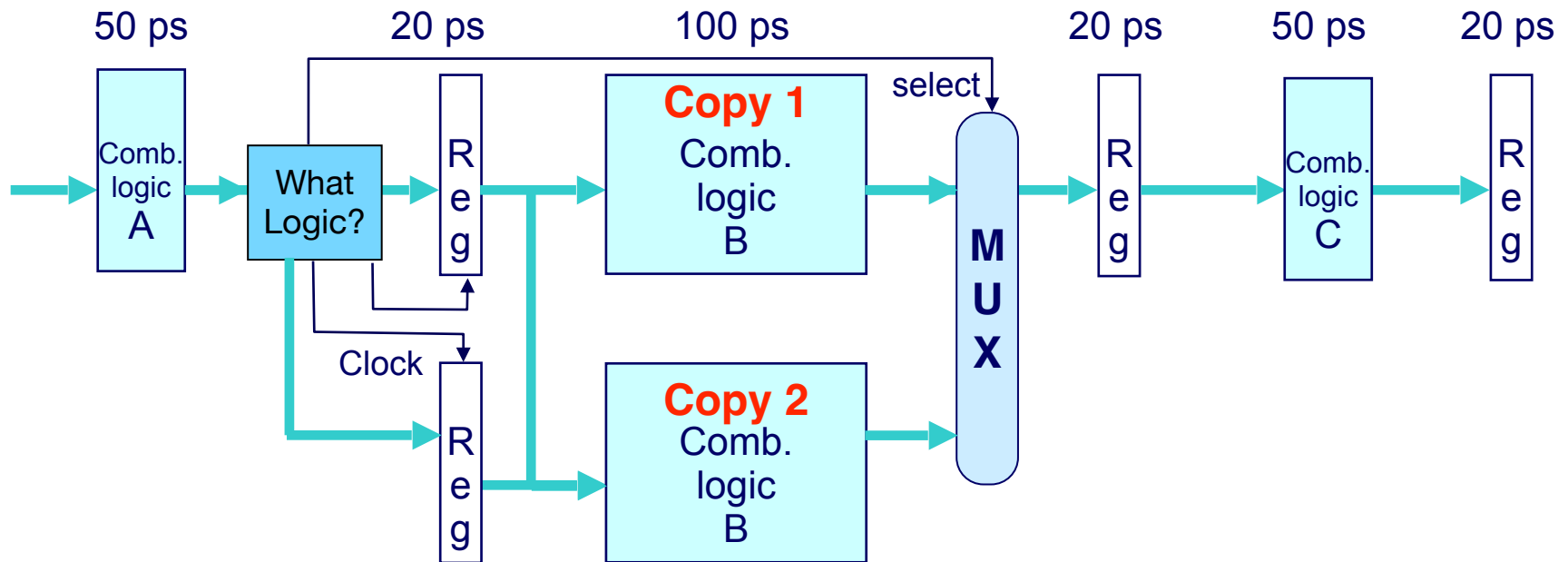
# Aside: Mitigating Unbalanced Pipeline

- Solution 1: Further pipeline the slow stages
  - Not always possible. What to do if we can't further pipeline a stage?
- Solution 2: Use multiple copies of the slow component




What logic do you need there?

Hint: it needs to control the clock signals of the two registers and the select signal of the MUX.
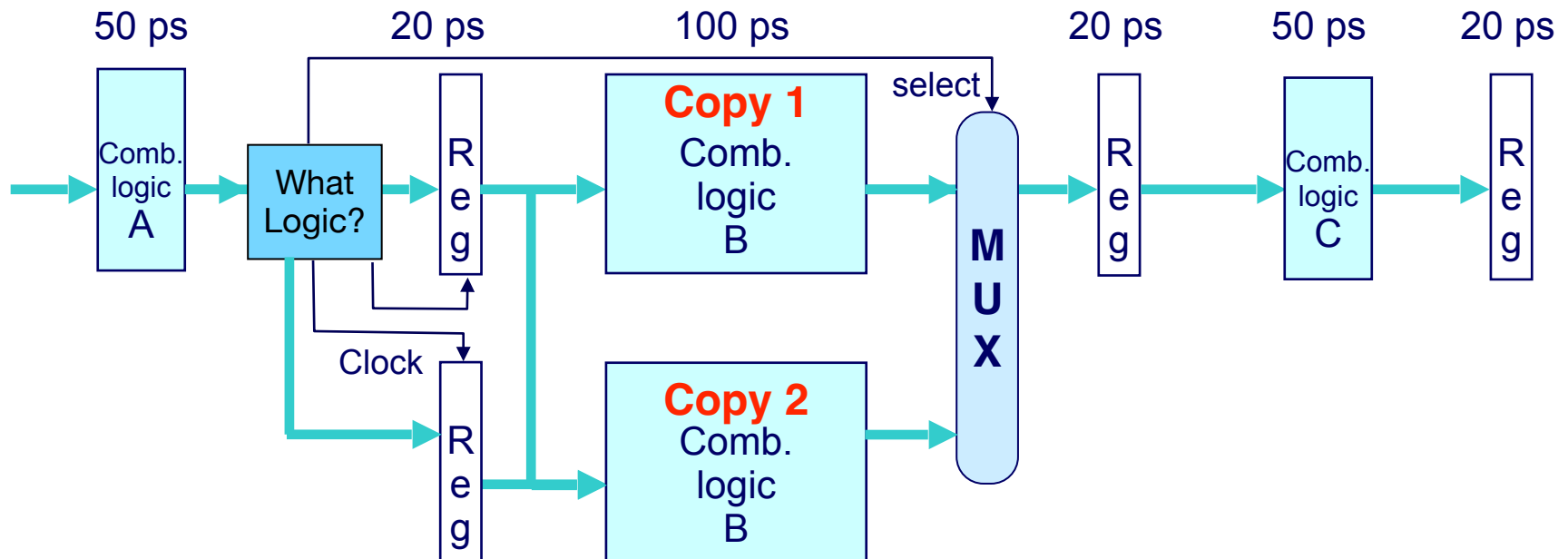
# Aside: Mitigating Unbalanced Pipeline

- Data sent to copy 1 in odd cycles and to copy 2 in even cycles.
- This is called 2-way interleaving. Effectively the same as pipelining Comb. logic B into two sub-stages.
- The cycle time is reduced to 70 ps (as opposed to 120 ps) at the cost of extra hardware.





# Another Way to Look At the Microarchitecture

## Principles:

- Execute each instruction one at a time, one after another
- Express every instruction as series of **simple steps**
- Dedicated hardware structure for completing each step
- Follow same general flow for each instruction type

**Fetch:** Read instruction from instruction memory


**Decode:** Read program registers

**Execute:** Compute value or address

**Memory:** Read or write data

**Write Back:** Write program registers

**PC:** Update program counter

 

## Fetch

- Read instruction from instruction memory

## Decode

- Read program registers

## Execute

- Compute value or address

## Memory

- Read or write data

## Write Back

- Write program registers

## PC

- Update program counter

# Stage Computation: Arith/Log. Ops



	OPq rA, rB	
Fetch	icode:ifun $\leftarrow M_1[PC]$	Read instruction byte
	rA:rB $\leftarrow M_1[PC+1]$	Read register byte
	valP $\leftarrow PC+2$	Compute next PC
Decode	valA $\leftarrow R[rA]$	Read operand A
	valB $\leftarrow R[rB]$	Read operand B
Execute	valE $\leftarrow \text{valB OP valA}$	Perform ALU operation
	Set CC	Set condition code register
Memory		
Write back	R[rB] $\leftarrow \text{valE}$	Write back result
PC update	PC $\leftarrow \text{valP}$	Update PC

# Stage Computation: `rmmovq`

`rmmovq rA, D(rB)`



	<code>rmmovq rA, D(rB)</code>	
Fetch	$\text{icode:ifun} \leftarrow M_1[\text{PC}]$ $\text{rA:rB} \leftarrow M_1[\text{PC}+1]$ $\text{valC} \leftarrow M_8[\text{PC}+2]$ $\text{valP} \leftarrow \text{PC}+10$	Read instruction byte Read register byte Read displacement D Compute next PC
Decode	$\text{valA} \leftarrow R[\text{rA}]$ $\text{valB} \leftarrow R[\text{rB}]$	Read operand A Read operand B
Execute	$\text{valE} \leftarrow \text{valB} + \text{valC}$	Compute effective address
Memory	$M_8[\text{valE}] \leftarrow \text{valA}$	Write value to memory
Write back		
PC update	$\text{PC} \leftarrow \text{valP}$	Update PC

# Stage Computation: Jumps

	jXX Dest	
Fetch	$\text{icode:ifun} \leftarrow M_1[\text{PC}]$	Read instruction byte
	$\text{valC} \leftarrow M_8[\text{PC}+1]$	Read destination address
	$\text{valP} \leftarrow \text{PC}+9$	Fall through address
Decode		
Execute	$\text{Cnd} \leftarrow \text{Cond}(\text{CC}, \text{ifun})$	Take branch?
Memory		
Write back		
PC update	$\text{PC} \leftarrow \text{Cnd} ? \text{valC} : \text{valP}$	Update PC

- Compute both addresses
- Choose based on setting of condition codes and branch condition

# Pipeline Stages

## Fetch

- Select current PC
- Read instruction
- Compute incremented PC

## Decode

- Read program registers

## Execute

- Operate ALU

## Memory

- Read or write data memory

## Write Back

- Update register file

